


# MECH366 : Modeling of Mechatronic Systems

## L9 : Modeling of electrical systems

Dr. Ryozo Nagamune  
Department of Mechanical Engineering  
University of British Columbia
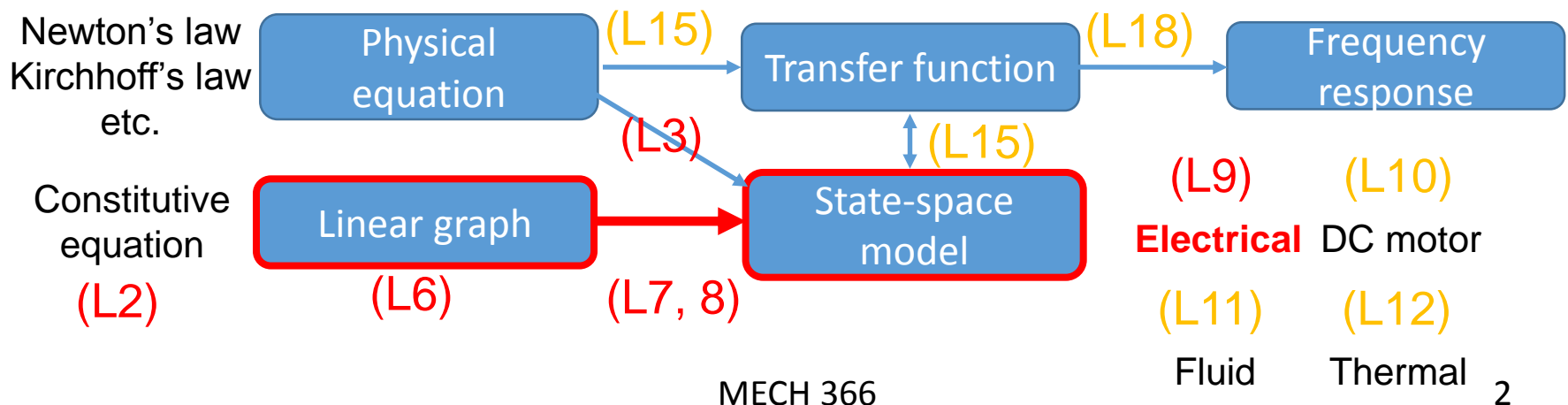
# Review and today's topic

- Up to now, we have studied for mechanical systems
  - How to draw linear graphs
  - How to derive state-space models from linear graphs
- Today, we will study modeling of electrical systems.
- Various models and their relations



# \_\_\_ : State variable

Constitutive relation for



System type	Energy storage element		Energy dissipating element
	A-Type	T-Type	D-Type
<b>Mechanical</b> (translational)	Mass	Spring	Viscous Damper
$v$ : velocity <b>across var.</b>	$m\dot{v} = f$	$\dot{f} = kv$	$f = bv$
$f$ : force <b>through var.</b>	$m$ : mass	$k$ : stiffness	$b$ : damping const.
<b>Electrical</b>	Capacitor	Inductor	Resistor
$v$ : voltage <b>across var.</b>	$C\dot{v} = i$	$L\dot{i} = v$	$v = Ri$
$i$ : current <b>through</b>	$C$ : capacitance	$L$ : inductance	$R$ : resistance
<b>Thermal</b>	Thermal capacitor	None	Thermal resistor
$T$ : temperature	$C_t\dot{T} = Q$		$T = R_tQ$
$Q$ : heat transfer rate	$C$ : thermal capacitance		$R_t$ : thermal resistance
<b>Fluid</b>	Fluid capacitor	Fluid inductor	Fluid resistor
$P$ : pressure difference	$C_f\dot{P} = Q$	$I_f\dot{Q} = P$	$P = R_fQ$
$Q$ : volume flow rate	$C_f$ : fluid capacitance	$I_f$ : fluid inductance	$R_f$ : fluid resistance

power

$$\mathcal{P} = fv$$

$$\mathcal{P} = iv$$



# Energy expressions based on across and through variables

	A-type element	T-type element
Mechanical $v$ : Across variable $f$ : Through variable	Kinetic energy $\frac{1}{2}mv^2$	Potential energy $\left(\frac{1}{2}kx^2 =\right) \frac{1}{2}\frac{f^2}{k}$
Electrical $v$ : Across variable $i$ : Through variable	Electrostatic energy $\frac{1}{2}Cv^2$	Electromagnetic energy $\frac{1}{2}Li^2$
Thermal $T$ : Across variable $Q$ : Through variable	Thermal energy $\int Q = C_t T$	N/A
Fluid $P$ : Across variable $Q$ : Through variable	Potential energy $\frac{1}{2}C_f P^2$	Kinetic energy $\frac{1}{2}I_f Q^2$


# Linear graph representation

- Single-port elements
  - Energy storage elements
  - Energy dissipation elements
  - Energy sources
- Two-port elements (Energy transfer elements)
  - Transformer
  - (Gyrator)

# Linear graph representation


## Electrical single-port elements

Energy storage element

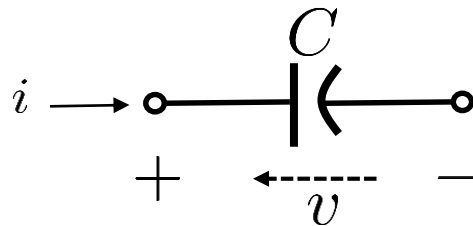


$$C \quad i, v \quad \dot{v} = \frac{1}{C} i$$

Energy storage element

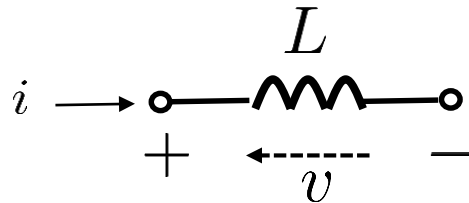

$$L \quad i, v \quad \dot{i} = \frac{1}{L} v$$

Energy dissipation element

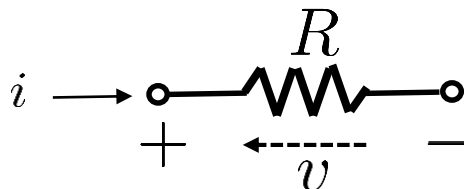

$$R \quad i, v \quad v = Ri$$


# Linear graph representation

- Single-port elements
  - Energy storage elements
  - Energy dissipation elements
  - Energy sources
- Two-port elements (Energy transfer elements)
  - Transformer
  - (Gyrator)


# Linear graph representation

## Electrical energy sources


- Current source

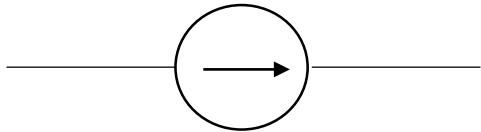


Linear graph

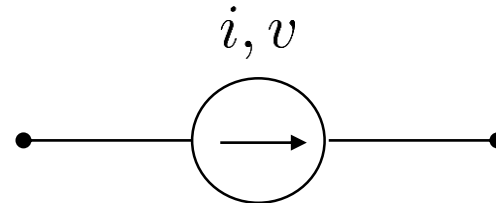

- Voltage source

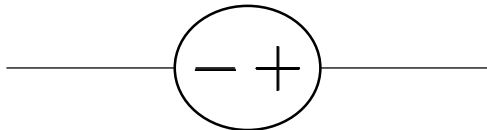

Linear graph

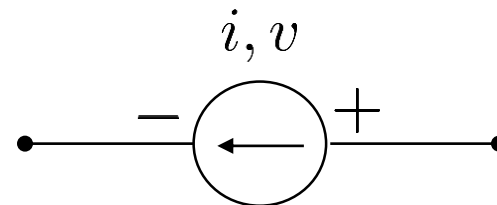




# Linear graph representation

- Single-port elements
  - Energy storage elements
  - Energy dissipation elements
  - Energy sources
- Two-port elements (Energy transfer elements)
  - Transformer
  - (Gyrator)
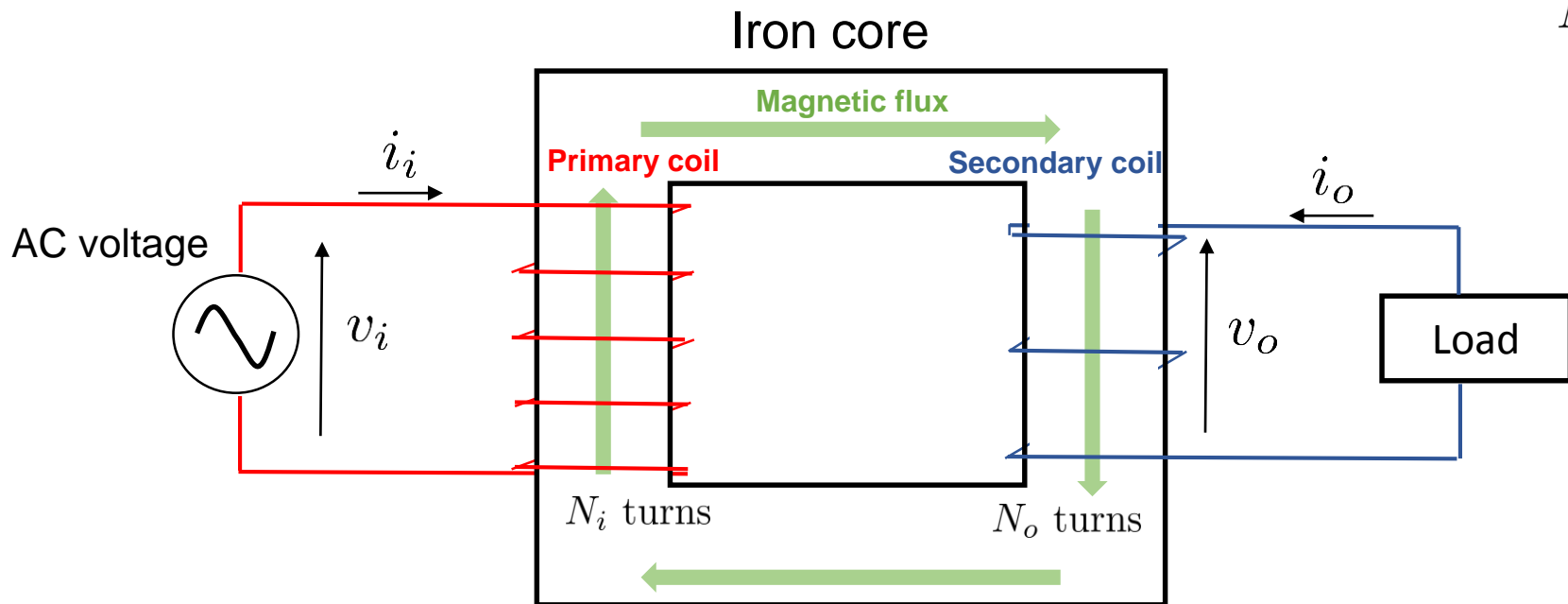
# Electrical transformer


- Passive device to step-up or step-down AC voltage.  
 $(r > 1)$                        $(r < 1)$

$$\text{Coil turn ratio } r := \frac{N_o}{N_i}$$


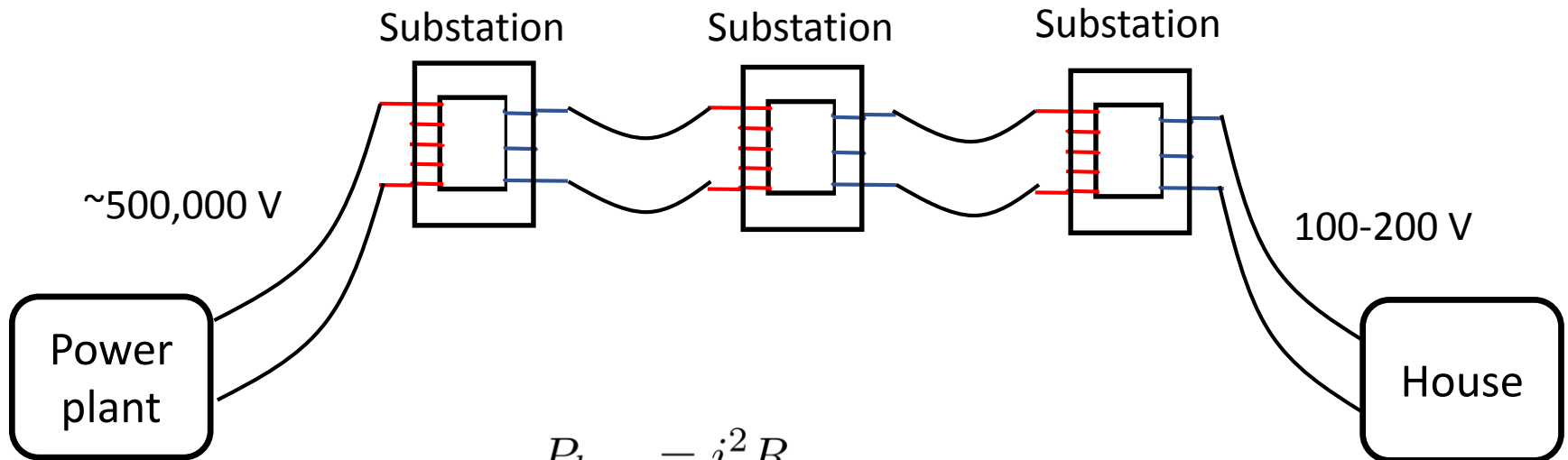
# Usage of electric transformer

Substations have electric transformers, to transform AC voltage from high to low, or low to high



$$P_{loss} = i^2 R$$

To reduce power heat losses during the transmission, power is sent with high voltage (small current).


# Linear graph representation

## Two-port element: Transformer


- Voltage ratio  $v_o = r v_i$
- Conservation of power

$$i_i v_i + i_o v_o = 0$$
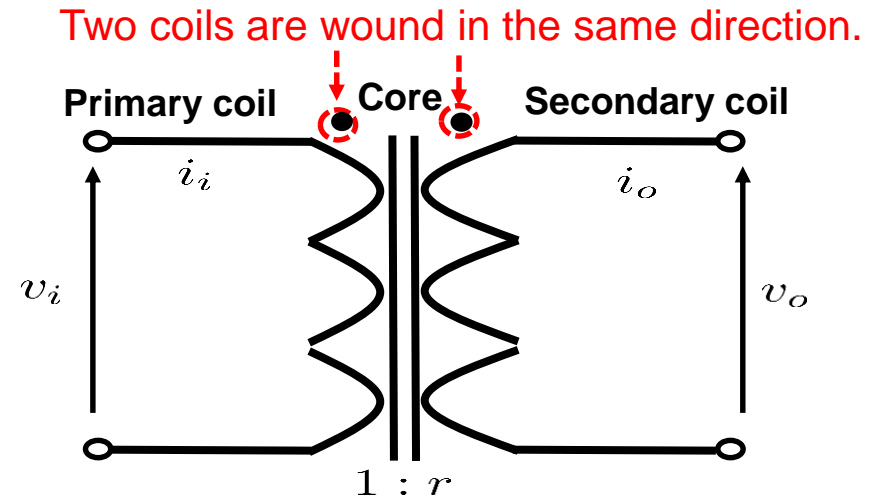
$$\rightarrow i_o = -\frac{v_i}{v_o} i_i = -\frac{1}{r} i_i$$



Linear graph

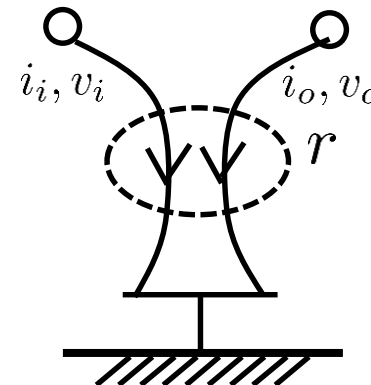


$$v_o = r v_i$$

$$i_o = -\frac{1}{r} i_i$$

# Example: RLC circuit (series)

- Circuit diagram

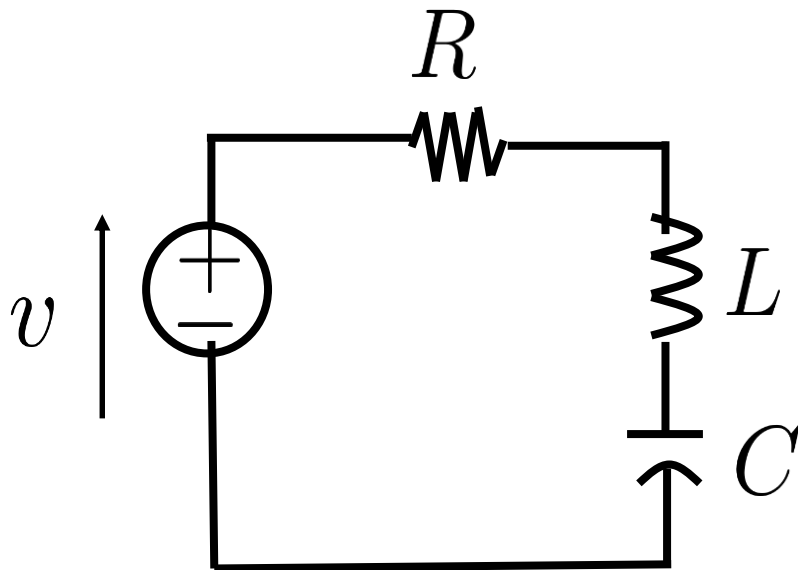



# Example: RLC circuit (series) (cont'd)


- Linear graph drawing
- State variable selection
- Loop & node equations
- State equation

Take a node for each  
different voltage point.

Direct all arrows on passive  
elements away from sources and  
toward the reference node.

# Example: RLC circuit (parallel)

- Circuit diagram

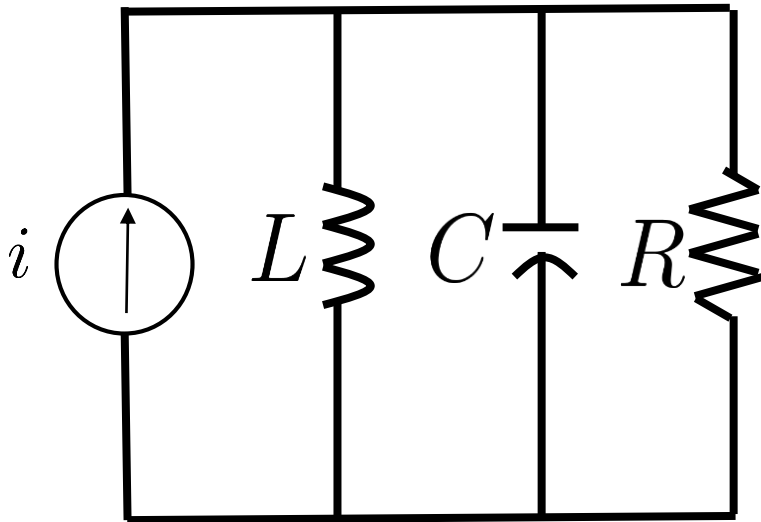

# Example: RLC circuit (parallel) (cont'd)


- Linear graph drawing
- State variable selection
- Loop & node equations
- State equation

Take a node for each  
different voltage point.

Direct all arrows on passive  
elements away from sources and  
toward the reference node.



# An exercise

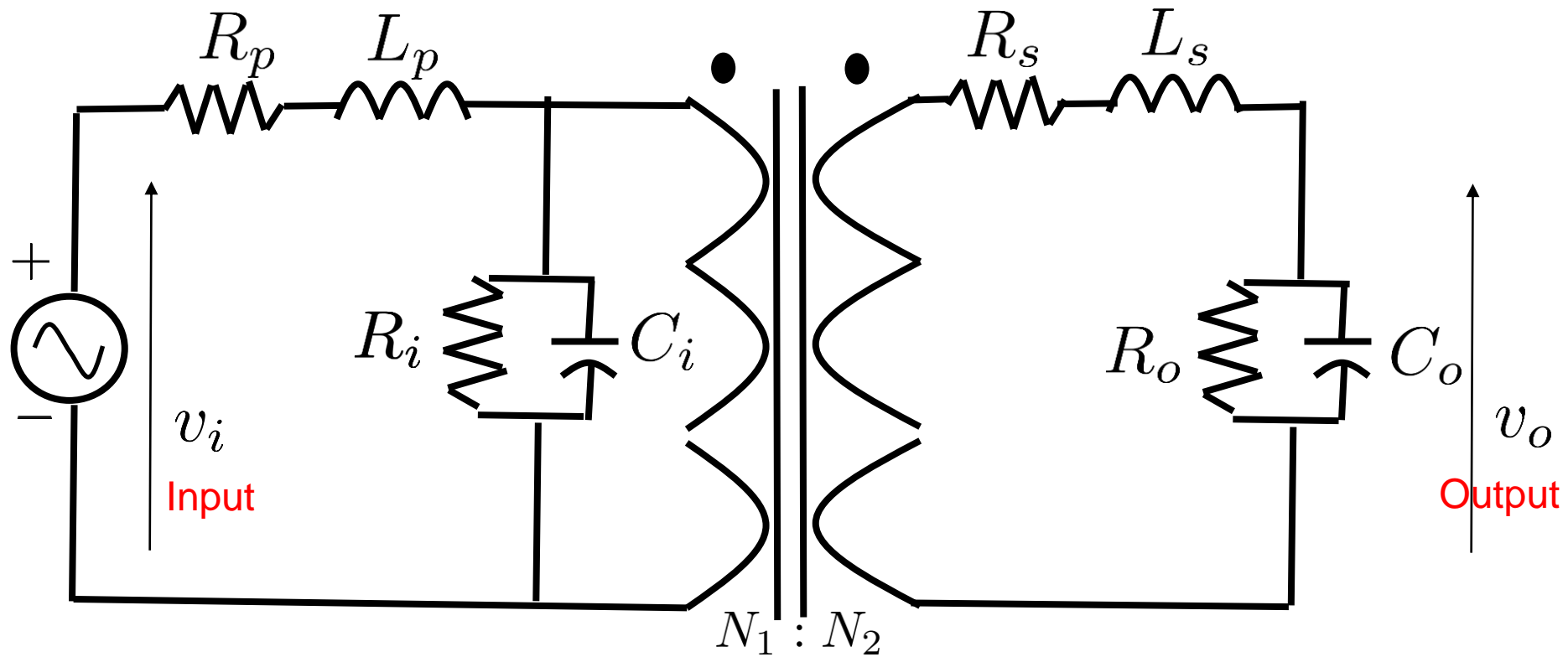



# Summary

- Linear graph for electrical systems
  - Single-port elements
    - Energy storage elements
    - Energy dissipation elements
    - Energy sources
  - Two-port elements (Energy transfer elements)
    - Transformer
    - (Gyrator)
- Derivation of state-space models from linear graphs
- **Homework 3:** Due Oct 7 (Monday), 3pm