



University of British Columbia
Electrical and Computer Engineering
Introduction to Microcomputers EECE259

Lecture 11: Finite State Machines.

Dr. Jesús Calviño-Fraga. P.Eng.
Department of Electrical and Computer Engineering, UBC
Office: KAIS 3024
E-mail: jesusc@ece.ubc.ca
Phone: (604)-827-5387

February 14/16, 2017

Copyright © 2009-2017, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Objectives

- Finite State Machines:
 - Types
 - State Diagram
 - State Table
 - Equations
 - Circuit
- Finite State Machines in VHDL
- Programmable State Machine

Lecture 11: Finite State Machines.

2

Copyright © 2009-2017, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Finite State Machines


- Finite State Machines (FSM) are a mathematical abstraction used to design sequential logic circuits as well as to write computer programs.
- In the previous lecture we studied synchronous counters. They are FSMs! The out of each state in a counter is the number of the state.
- There are two kinds of FSMs:
 - FSMs whose outputs are only a function of the current state. They are known as Moore FSMs. They are synchronous FSMs. The synchronous counters we studied in the previous lecture are all Moore FSMs.
 - FSMs whose outputs are a both a function of the current state and the inputs. They are know as Mealy FSMs they are asynchronous FSMs.
- The design of FSMs is very similar to the design of arbitrary count synchronous counters.

Lecture 11: Finite State Machines.

3

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Mealy Type FSM

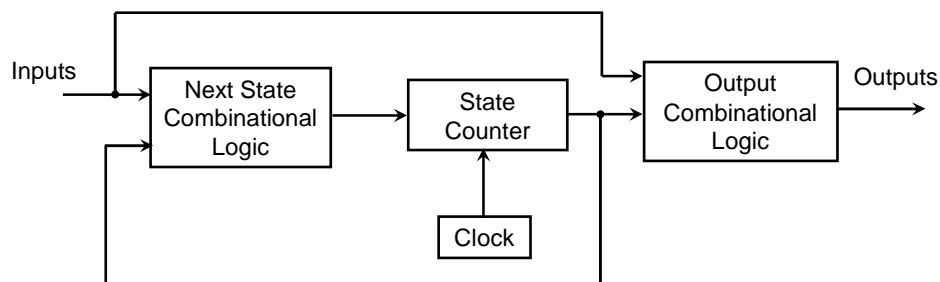


Lecture 11: Finite State Machines.

4

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Moore Type FSM

 

Lecture 11: Finite State Machines.


5

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Design Example 1

- Design a FSM that controls the automatic coffee dispenser shown below

Hot Chocolate

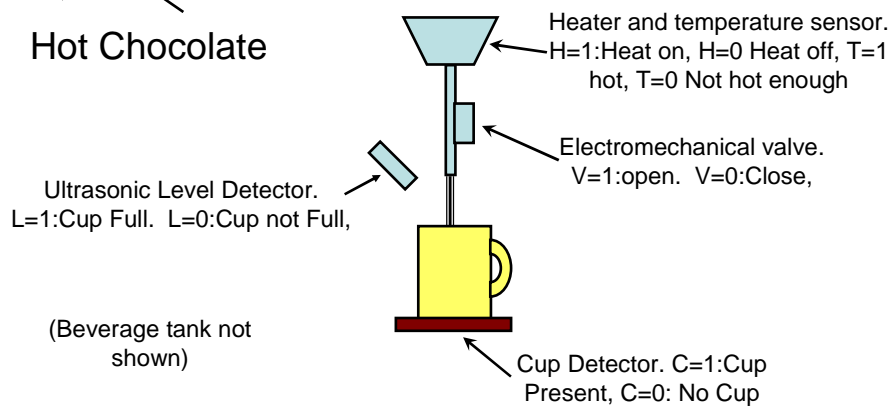


Lecture 11: Finite State Machines.

6

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

State Diagram

C: Cup sensor
L: Cup Full sensor
V: Valve on/off
H: Heater on/off
T: Temperature sensor

 


Lecture 11: Finite State Machines.

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

7

State Table

Inputs			State		Next		Output s	
C	L	T	Q ₁	Q ₀	D ₁	D ₀	H	V
0	X	X	0	0	0	0	0	0
1	X	X	0	0	0	1	0	0
0	X	X	0	1	0	0	1	0
1	X	0	0	1	0	1	1	0
1	X	1	0	1	1	0	1	0
0	X	X	1	0	0	0	0	1
1	0	X	1	0	1	0	0	1
1	1	X	1	0	1	1	0	1
0	X	X	1	1	0	0	0	0
1	X	X	1	1	1	1	0	0

 

Lecture 11: Finite State Machines.

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

8

Get Equations

$$D_1 = C.T.Q'_1.Q_0 + C.L'.Q_1.Q'_0 + C.L.Q_1.Q'_0 + C.Q_1.Q_0 =$$

$$D_1 = C.T.Q'_1.Q_0 + C.Q_1.Q'_0 + C.Q_1.Q_0 =$$

$$D_1 = C.T.Q'_1.Q_0 + C.Q_1 =$$

$$D_1 = C.(T.Q'_1.Q_0 + Q_1)$$

$$D_0 = C.Q'_1.Q'_0 + C.T'.Q'_1.Q_0 + C.L.Q_1.Q'_0 + C.Q_1.Q_0 =$$

$$D_0 = C.(Q'_1.Q'_0 + T'.Q'_1.Q_0 + L.Q_1.Q'_0 + Q_1.Q_0)$$

$$H = Q'_1.Q_0$$


$$V = Q_1.Q'_0$$

Lecture 11: Finite State Machines.

9

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Draw the Circuit

 

Lecture 11: Finite State Machines.

10

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Designing Finite State Machines

- Understand specifications
- Derive state diagram
- Create state table
- Perform state minimization (if necessary)
- Encode states (state assignment)
- Create state-assigned table
- Select type of Flip-Flop to use
- Determine Flip-Flop input equations and FSM output equations.
- Draw circuit diagram

Lecture 11: Finite State Machines.

11

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

VHDL Finite State Machines


- Nowadays it is very easy to implement FSMs.
- VHDL has facilities to easily implement them.
- Quartus Prime goes even farther: it has templates for FSM in Mealy and Moore configurations!

Lecture 11: Finite State Machines.

12

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

VHDL Finite State Machines

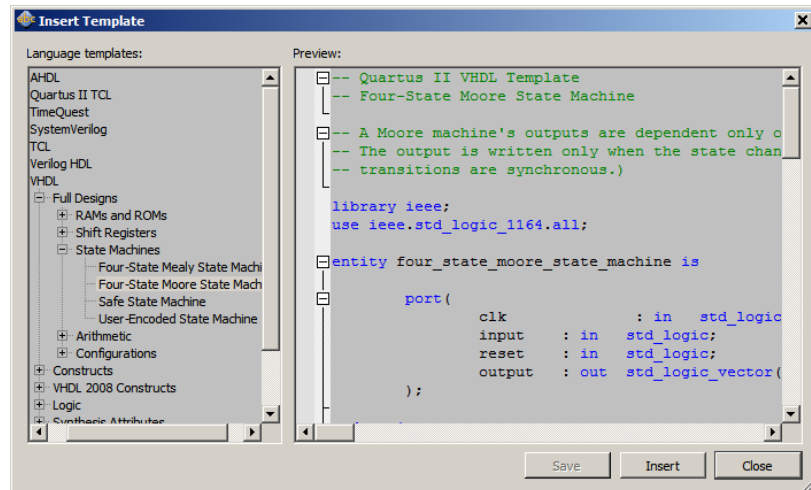

Lecture 11: Finite State Machines.

13

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

VHDL FSM

```
-- Quartus II VHDL Template
-- Four-State Moore State Machine

-- A Moore machine's outputs are dependent only on the current state.
-- The output is written only when the state changes. (State
-- transitions are synchronous.)

library ieee;
use ieee.std_logic_1164.all;

entity fsm1 is

    port(
        clk, reset      : in  std_logic;
        Cup, Level, Temperature : in  std_logic;
        Ready            : out std_logic;
        Heater, Valve    : out std_logic
    );

end entity;
```

Lecture 11: Finite State Machines.

14

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

VHDL FSM

```
architecture rtl of fsm1 is

    -- Build an enumerated type for the state machine
    type state_type is (s0, s1, s2, s3);

    -- Register to hold the current state
    signal state : state_type;

begin
```

Lecture 11: Finite State Machines.

15

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

VHDL FSM

```
-- Logic to advance to the next state
process (clk, reset)
begin
    if reset = '0' then
        state <= s0;
    elsif (rising_edge(clk)) then
        case state is
            when s0=>
                if Cup = '1' then
                    state <= s1;
                else
                    state <= s0;
                end if;
            when s1=>
                if Cup = '0' then
                    state <= s0;
                elsif Temperature = '1' then
                    state <= s2;
                else
                    state <= s1;
                end if;
        end case;
    end if;
end process;
```

Lecture 11: Finite State Machines.

16

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

VHDL FSM

```
when s2=>
  if Cup = '0' then
    state <= s0;
  elsif Level = '1' then
    state <= s3;
  else
    state <= s2;
  end if;
when s3 =>
  if Cup = '0' then
    state <= s0;
  else
    state <= s3;
  end if;
end case;
end if;
end process;
```

Lecture 11: Finite State Machines.

17

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

VHDL FSM

```
-- Output depends solely on the current state
process (state)
begin
  case state is
    when s0 =>
      Ready <= '1';
      Heater <= '0';
      Valve <= '0';
    when s1 =>
      Ready <= '0';
      Heater <= '1';
      Valve <= '0';
    when s2 =>
      Ready <= '0';
      Heater <= '0';
      Valve <= '1';
    when s3 =>
      Ready <= '0';
      Heater <= '0';
      Valve <= '0';
  end case;
end process;

end rtl;
```

Lecture 11: Finite State Machines.

18

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Pin Assignments in DE0-CV Board


Signal Name	DE0-CV Board Name	FPGA Pin #
clk	50 MHz Clock	PIN_M9
reset	KEY0 (active low!)	PIN_U7
Cup	SW0	PIN_U13
Level	SW1	PIN_V13
Temperature	SW2	PIN_T13
Ready	LEDR0	PIN_AA2
Heater	LEDR1	PIN_AA1
Valve	LEDR2	PIN_W2

Lecture 11: Finite State Machines.

19

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 2: Simple Elevator

 

- M_U and M_D make the elevator go up or down.
- S_1 and S_2 detect if the elevator is in floor one or two
- B_1 and B_2 are used to call the elevator to each floor
- B_E is used to make the elevator move to the other floor.


After Reset the elevator is in the bottom floor

Lecture 11: Finite State Machines.

20

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 2: Simple Elevator

 

Lecture 11: Finite State Machines.

21

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 2: State Table

B_1+B_E	B_2+B_E	S_1	S_2	Q_1	Q_0	D_1	D_0	M_U	M_D
X	0	X	X	0	0	0	0	0	0
X	1	X	X	0	0	0	1	0	0
X	X	X	0	0	1	0	1	1	0
X	X	X	1	0	1	1	0	1	0
0	X	X	X	1	0	1	0	0	0
1	X	X	X	1	0	1	1	0	0
X	X	0	X	1	1	1	1	0	1
X	X	1	X	1	1	0	0	0	1

$$D_1 = S_2 \cdot Q_1' \cdot Q_0 + (B_1+B_E)' \cdot Q_1 \cdot Q_0' + (B_1+B_E) \cdot Q_1 \cdot Q_0' + S_1' \cdot Q_1 \cdot Q_0$$

$$D_0 = (B_2+B_E) \cdot Q_1' \cdot Q_0' + S_2' \cdot Q_1' \cdot Q_0 + (B_1+B_E) \cdot Q_1 \cdot Q_0' + S_1' \cdot Q_1 \cdot Q_0$$

$$M_U = Q_1' \cdot Q_0$$

$$M_D = Q_1 \cdot Q_0$$

Circuit is exercise
at the end!

Lecture 11: Finite State Machines.

22

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Programmable State Machine


- From the previous examples notice that the hardware implementations of FSMs may get very complex.
- For large FSM it takes a long time to design and assemble.
- An alternative is to use VHDL, but we are just moving the problem from one technology to another.
- A better option is to have a FSM that is easy to design with and easy to setup.
- A programmable state machine is both easy to design with and setup. It is the direct ancestor of modern processors!

Lecture 11: Finite State Machines.

23

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Programmable State Machine

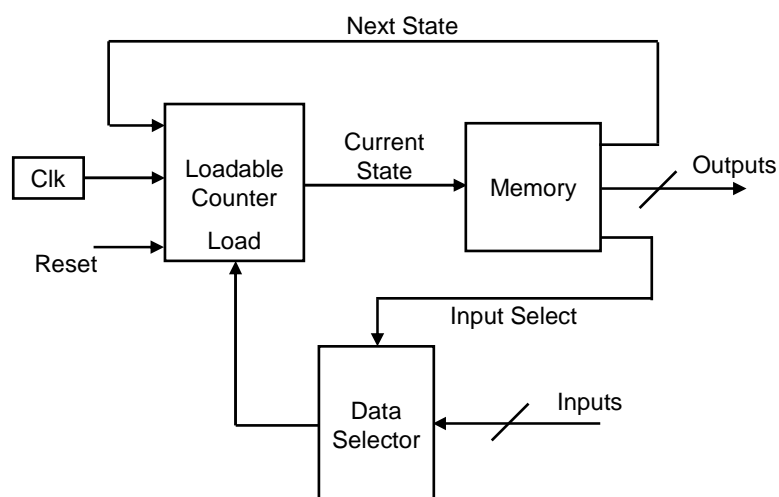

Lecture 11: Finite State Machines.

24

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Memory


- Typically, memory has the following signals:
 - An address bus. This allows us to select each particular memory location.
 - A data bus. Here is where we put the information to be stored to the memory, or where we get the information previously stored.
 - A control bus. These are the signals that tell the memory to write, read, or disable/enable the whole memory.

Lecture 11: Finite State Machines.

25

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Random Access Memory (RAM)

 

CY62256N

256K (32K x 8) Static RAM

Address Bus: Signals A₀ to A₁₄. Since we have 15 address signals, the memory has $2^{15}=32768$ locations.

Data Bus: Signals I/O₀ to I/O₇. It is an 8-bit data bus.

Control Bus: Signals CE*, OE*, and WE*.

CE*: Enables this IC for read or write.

OE*: Makes the data bus an output. Read from memory.


WE*: Makes the data bus an input. Write to memory

Lecture 11: Finite State Machines.


26

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Read Only Memory (ROM)

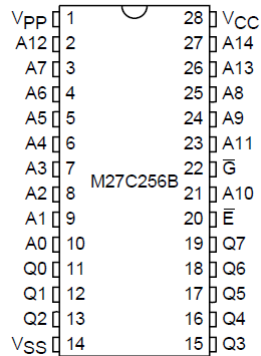

 256 Kbit (32Kb × 8) UV EPROM
(Ultra Violet Electrically
Programmable Read Only
Memory)



Address Bus: Same as previous slide.

Data Bus: Signals Q_0 to Q_7 .

Control Bus: Signals E^* , G^* , and VPP .

E^* : Enables this IC for read.

G^* : Makes the data bus an output.


VPP : Voltage (12.5V) used to write to the memory using an external programmer.

Lecture 11: Finite State Machines.

27

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Loadable Counter

 

74HC161 4-bit
synchronous binary
counter

The '161 is one of many counters available. Not happy with this counter? Design your own using flip-flops or VHDL!

According to the datasheet, to count: ENT, ENP, $LOAD^*$, and CLR^* must be '1'.

When $LOAD^*=0$, the current count is set to whatever is in inputs A to D.


Signals RCO, ENT, and ENP are used to connect several chips together to make a bigger counter (8-bits, for example)

Lecture 11: Finite State Machines.

28

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Data Selector

 

74HC151 8 to 1 data selector

FUNCTION TABLE					
INPUTS				OUTPUTS	
SELECT			STROBE \overline{G}	Y	W
C	B	A			
X	X	X	H	L	H
L	L	L	L	D0	$\overline{D0}$
L	L	H	L	D1	$\overline{D1}$
L	H	L	L	D2	$\overline{D2}$
L	H	H	L	D3	$\overline{D3}$
H	L	L	L	D4	$\overline{D4}$
H	L	H	L	D5	$\overline{D5}$
H	H	L	L	D6	$\overline{D6}$
H	H	H	L	D7	$\overline{D7}$

D0, D1 . . . D7 = the level of the respective D input


Lecture 11: Finite State Machines.

29


Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Clock Generation

 Old good LM555 IC in A-stable configuration!



Output at pin 3

 


$$f = \frac{1.44}{(R_A + 2R_B)C}$$

Lecture 11: Finite State Machines.

30

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM: Simulation using Multisim

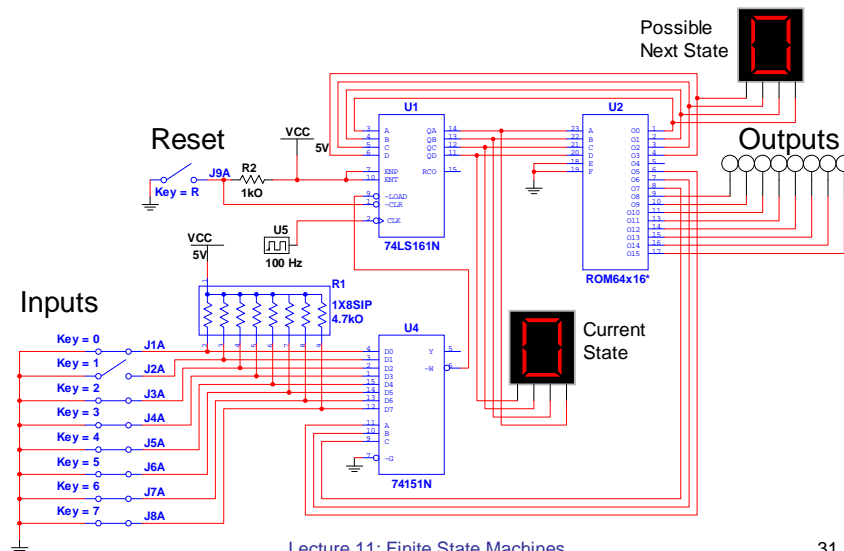

Lecture 11: Finite State Machines.

31

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM: Simulation using Multisim

- The program is stored in the 64x16 ROM (64 words, 16-bit each).
- To change the program in Multisim, double click the memory, then click “Edit Model”.
- Modify the output of the memory for each location according to your program. Then click “Change part model”, followed by Ok.
- To simulate the Programmable State Machine press F5.

Lecture 11: Finite State Machines.

32

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM: Operation Code

- Each instruction in our programmable state machine consist of 16-bits with the following meanings:

Q15	Q14	Q13	Q12	Q11	Q10	Q9	Q8	Q7	Q6	Q5	Q4	Q3	Q2	Q1	Q0
U7	U6	U5	U4	U3	U2	U1	U0	IC	IB	IA	X	ND	NC	NB	NA

General purpose outputs Input select Possible next state, depending of input


Lecture 11: Finite State Machines.

33

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM Example

- Program the following state diagram:

 


Lecture 11: Finite State Machines.

34

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM Example

- Some observations:
 - State 2 increments unconditionally to state 3. Therefore we need to force an input to always zero. Say it is input zero.
 - State 3 jumps unconditionally to state 0. Therefore we need to force an input to always one. Say it is input one.
 - State 1 jumps if the condition is zero. Our PSM can jump only with one. We can solve this in different ways as outlined in the next slide.

 


Lecture 11: Finite State Machines.

35

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM: How to jump when an input is zero.

- Use an inverter (NOT gate) connected to an extra input.
- Add an extra state:

 


Lecture 11: Finite State Machines.

36

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM with converted state

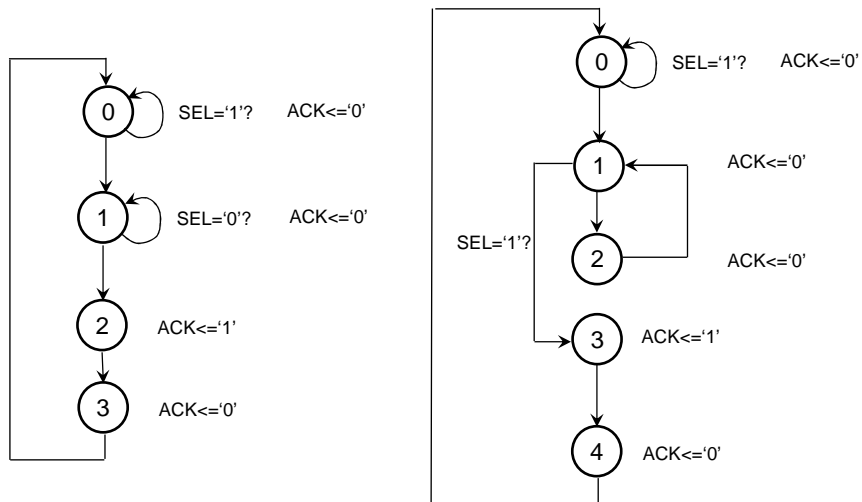

Lecture 11: Finite State Machines.

37

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM: Signal Assignments

Signal	PSM
'0'	Input 0 ($I_A=0, I_B=0, I_C=0$)
'1'	Input 1 ($I_A=1, I_B=0, I_C=0$)
'SEL'	Input 2 ($I_A=0, I_B=1, I_C=0$)
'ACK'	Output 0 (U0)


Lecture 11: Finite State Machines.

38

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

PSM Code

State				Outputs								Input select			Next State					
D	C	B	A	U ₇	U ₆	U ₅	U ₄	U ₃	U ₂	U ₁	U ₀	I _C	I _B	I _A	X	N _D	N _C	N _B	N _A	
0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	X	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0	X	0	0	1	1
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	X	0	0	0	1
0	0	1	1	0	0	0	0	0	0	0	1	0	0	0	0	X	X	X	X	X
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	X	0	0	0	0


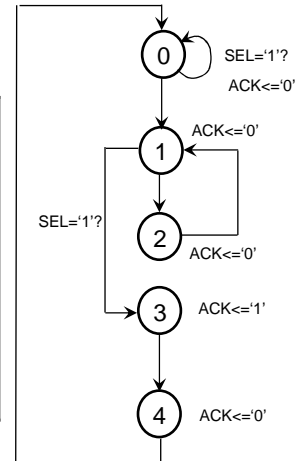


Lecture 11: Finite State Machines.

39

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Simple Elevator using PSM

  

Lecture 11: Finite State Machines.

40

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Simple Elevator using PSM

Signal	PSM
0	Input 0
1	Input 1
B_1+B_E	Input 2
B_2+B_E	Input 3
S_1	Input 4
S_2	Input 5
M_U	Output 0 (U0)
M_D	Output 1 (U1)

Pin Assignments

Lecture 11: Finite State Machines.


41

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Simple Elevator using PSM

B_1+B_E Input 2
 B_2+B_E Input 3
 S_1 Input 4
 S_2 Input 5

D	C	B	A	U ₇	U ₆	U ₅	U ₄	U ₃	U ₂	M _D	M _U	I _C	I _B	I _A	X	N _D	N _C	N _B	N _A
0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	X	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	X	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0	1	1	0	1	X	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	1	0	0	1	X	0	0	1	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	X	0	1	1	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	X	0	1	0	0
0	1	1	0	0	0	0	0	0	0	1	0	1	0	0	X	0	0	0	0
0	1	1	1	0	0	0	0	0	0	1	0	0	0	1	X	0	1	1	0

 

Lecture 11: Finite State Machines.

42

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Exercises

1. Draw the circuit for example 2 given in class.
2. Write a VHDL program that implements the state diagram of example 2.
3. Solve example 1 using the PSM given in class.
4. Using a two input XOR gate and memory output 'U7', modify the PSM presented in this lecture so it can be programmed to jump either with zero or one.

Lecture 11: Finite State Machines.

43

Copyright © 2009-2017, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.