



University of British Columbia  
Electrical and Computer Engineering  
Digital Design and Microcomputers CPEN312

## Lecture 9: Flip-Flops and Registers.

Dr. Jesús Calviño-Fraga. P.Eng.  
Department of Electrical and Computer Engineering, UBC  
Office: KAIS 3024  
E-mail: [jesusc@ece.ubc.ca](mailto:jesusc@ece.ubc.ca)  
Phone: (604)-827-5387

February 2, 2017

Copyright © 2009-2016, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Objectives


- Latches
- Flip-Flops
- Registers
- Asynchronous/Ripple Counters
- Cascade Ripple Counters

Lecture 9: Flip-Flops and Registers

2

Copyright © 2009-2016, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.


## SR Latch With NOR Gates

 

S	R	Q	Q'
0	0	0/1	0/1
0	1	0	1
1	0	1	0
1	1	0	0

(no change)

Characteristic Table

 


Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

3

## SR Latch With NOR Gates

 


Time	R	S	Q	Q-bar	Comment
	0	0	?	?	Stored state unknown
	0	1	1	0	"Set" Q to 1
	0	0	1	0	Now Q "remembers" 1
	1	0	0	1	"Reset" Q to 0
	0	0	0	1	Now Q "remembers" 0
	1	1	0	0	Both go low (forbidden)
	0	0	?	?	Random!

Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

4

## SR Latch With NAND Gates

 


Time	R	S	Q	$\bar{Q}$	Comment
↓	1	1	?	?	Stored state unknown
	1	0	1	0	"Set" Q to 1
	1	1	1	0	Now Q "remembers" 1
	0	1	0	1	"Reset" Q to 0
	1	1	0	1	Now Q "remembers" 0
	0	0	1	1	Both go high
	1	1	?	?	Random!

Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

5

## Gated SR Latch

 


E	S	R	Q	Q'
1	1	0	1	0
1	0	1	0	1
1	0	0	Q(t-1)	Q'(t-1)
1	1	1	?	?
0	x	x	Q(t-1)	Q'(t-1)

Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

6

## Gated D Latch

 

E	S	R	Q	Q'
1	1	0	1	0
1	0	1	0	1
0	x	x	Q(t-1)	Q'(t-1)


The humble D Latch is the basic unit of memory! It can store just one bit.

Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

7

## Latch Symbols

 


Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

8

## Multi-bit D latch

- Used to store n-bits.

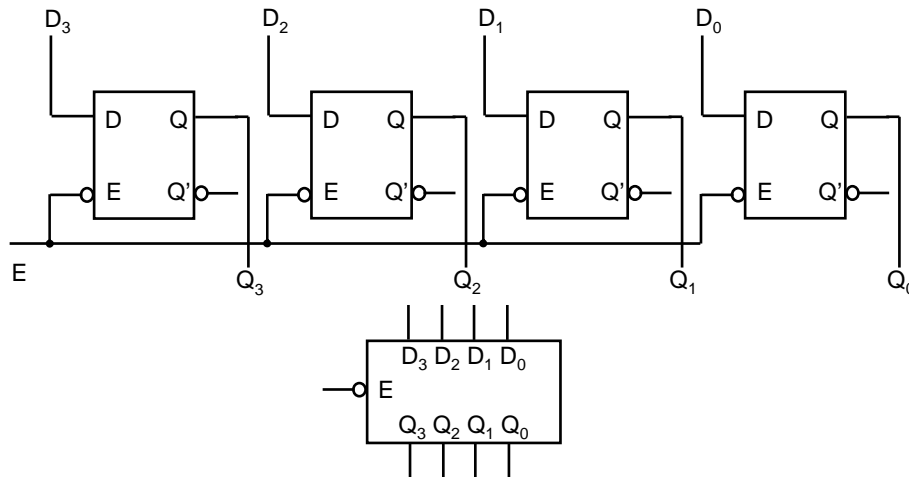


Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

9

## Improved D Latch

 


I mentioned before that the D latch is a unit of memory. Since we want to have as much memory as possible, we optimize its design as much as possible. By implementing the D latch as in the figure above we save one gate.

Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

10

## Gated D Latch with Output enable

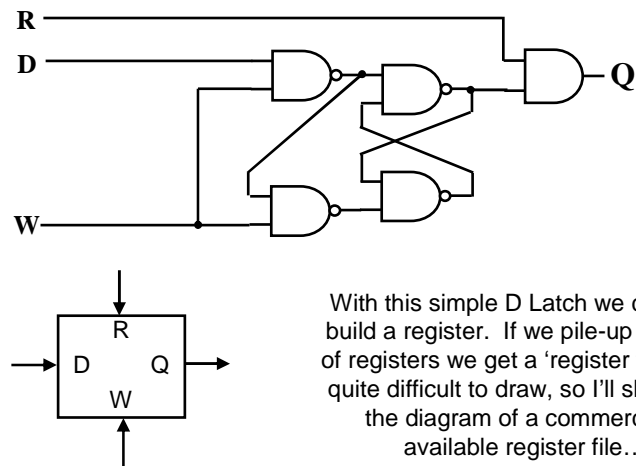

With this simple D Latch we can also build a register. If we pile-up a bunch of registers we get a 'register file'. It is quite difficult to draw, so I'll show you the diagram of a commercially available register file...


Lecture 9: Flip-Flops and Registers

11

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## 74LS670 register file

- Provides one input and one output port only:

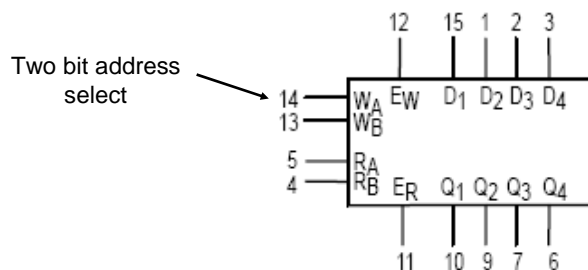


Lecture 9: Flip-Flops and Registers

12

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## 74LS670 register file

 

Lecture 9: Flip-Flops and Registers

13

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Example 1


- BCD Adder/Subtractor with latched input:
  - We can connect the same switches to both A and B.
  - Uses one 4-bit latch.
  - We need an “Enter” key to provide the value in port A throughout the latch.
  - Lab #2 can be done now with 4 BCD digits!

Lecture 9: Flip-Flops and Registers

14

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## BCD Adder/Subtractor

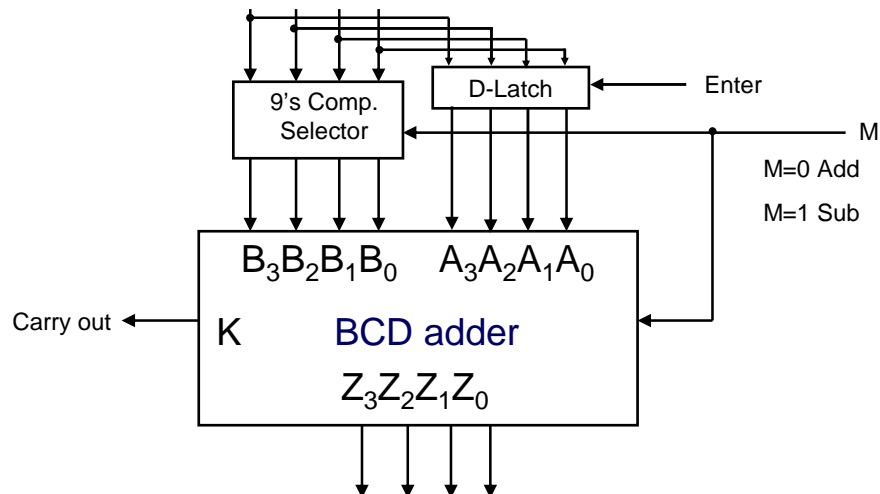

Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

15

## Limitations of Latch Circuits

- When the enable signal is active, the excitation inputs are gated directly to the output Q. Therefore, any change in the inputs causes an immediate change in the latch output.
- We can solve the problem above by using a special timing control signal: the *clock*. It restricts the times at which the states of the latch may change.
- The addition of the clock signal leads to the edge-triggered latch, also called *flip-flop*.

Lecture 9: Flip-Flops and Registers


Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

16



# Flip-flops

- In Flip-flops, the outputs change state at a specified point on an input called the *clock*.
- They can change state either at the *positive edge* (rising edge) or at the *negative edge* (falling edge) of the clock signal.

 


Lecture 9: Flip-Flops and Registers

17


Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.
 
# Flip-flops

- Symbols for the SR, D and JK edge-triggered flip-flops. Note the ">" symbol at the clock input.



Positive edge-triggered flip-flops

 


Negative edge-triggered flip-flops

Lecture 9: Flip-Flops and Registers

18

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## SR Flip-Flop

 

CLK	S	R	Q	Q'	Comment
?	0	0	Q(t-1)	Q'(t-1)	No Change
↑	0	1	0	1	Reset
↑	1	0	1	0	Set
↑	1	1	?	?	Invalid

? = irrelevant ("don't care")


↑ = clock transition LOW to HIGH

Lecture 9: Flip-Flops and Registers

19

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Clock Edge Detectors

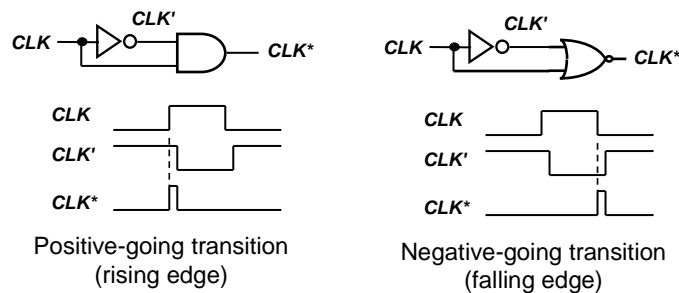


In both detectors above we use the delay introduced by the NOT gate to generate a very narrow output pulse!

Lecture 9: Flip-Flops and Registers

20

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## D Flip-flop

 

A positive edge-triggered D flip-flop formed with an S-R flip-flop.

D	CLK	Q(T+1)	Comment
1	↑	1	Set
0	↑	0	Reset

↑ = clock transition LOW to HIGH

Lecture 9: Flip-Flops and Registers

21

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## JK Flip-Flop


- Q and Q' are fed back to the pulse-steering NAND gates.
- No invalid state.
- The JK Flip-Flop includes a *toggle* state.
  - $J=HIGH$  (and  $K=LOW$ )  $\Rightarrow$  SET state
  - $K=HIGH$  (and  $J=LOW$ )  $\Rightarrow$  RESET state
  - both inputs LOW  $\Rightarrow$  no change
  - both inputs HIGH  $\Rightarrow$  toggle

Lecture 9: Flip-Flops and Registers

22

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

# JK Flip-Flop

 

J	K	CLK	Q(t+1)	Comments
0	0	↑	Q(t)	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	Q(t)'	Toggle

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


$$Q(t+1) = J \cdot Q' + K' \cdot Q$$

Lecture 9: Flip-Flops and Registers

23

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

# T Flip-Flop

 

T	CLK	Q(t+1)	Comments
0	↑	Q(t)	No change
1	↑	Q(t)'	Toggle


Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

Lecture 9: Flip-Flops and Registers


24

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Example: Frequency Division

 

Divide clock frequency by 2.

 

Divide clock frequency by 4.

This is also a counter!

Lecture 9: Flip-Flops and Registers

25

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Asynchronous Inputs: Preset & Clear


- SR, D and JK inputs are synchronous inputs, as data on these inputs are transferred to the flip-flop's output only on the sensitive edge of the clock pulse.
- Asynchronous inputs affect the state of the flip-flop independently of the clock; example: *preset (PRE)* and *clear (CLR)*. Assuming active high preset and clear inputs:
  - When  $PRE=HIGH$ , Q is immediately set to HIGH.
  - When  $CLR=HIGH$ , Q is immediately cleared to LOW.
- The flip-flop is in normal operation mode when both  $PRE$  and  $CLR$  inactive.

Lecture 9: Flip-Flops and Registers

26

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Asynchronous Inputs: Preset & Clear

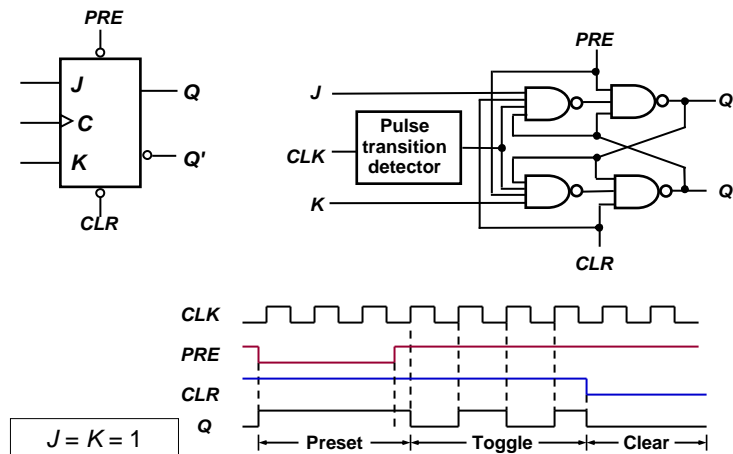


Lecture 9: Flip-Flops and Registers

27

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Master-Slave JK Flip-Flop

- Another way of implementing a Flip-Flop is by using a Master-Slave configuration. For example, this is the JK flip-flop:

 

Lecture 9: Flip-Flops and Registers

28

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Counters

- Counters are circuits that cycle through a specified number of states.
- Two types of counters:
  - synchronous (parallel) counters
  - asynchronous (ripple) counters
- Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- Synchronous counters apply the same clock to all flip-flops.

Lecture 9: Flip-Flops and Registers

29

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Ripple Counters

- Ripple counters: the flip-flops do not change their outputs at exactly the same time because they do not have a common clock source.
- Also known as asynchronous counters, as the input clock pulse propagates asynchronously through the counter. As a consequence accumulative delay is present and an important drawback.
- For  $n$  flip-flops  $\rightarrow$  a MOD (modulus)  $2^n$  counter. (For example for  $n=3$ , the counter has up to 8 possible 'count' values).
- Output of the last flip-flop (MSB) divides the input clock frequency by the MOD number of the counter, for this reason a counter is used also as a *frequency divider*.


Lecture 9: Flip-Flops and Registers

30

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Binary Ripple Counter

- Output of one flip-flop is connected to the clock input of the next flip-flop. If we use two F-Fs:

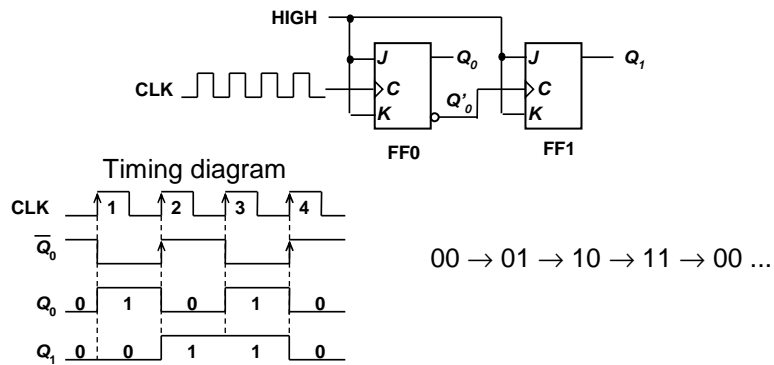


Lecture 9: Flip-Flops and Registers

31

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Binary Ripple Counter

- If we use three F-Fs:

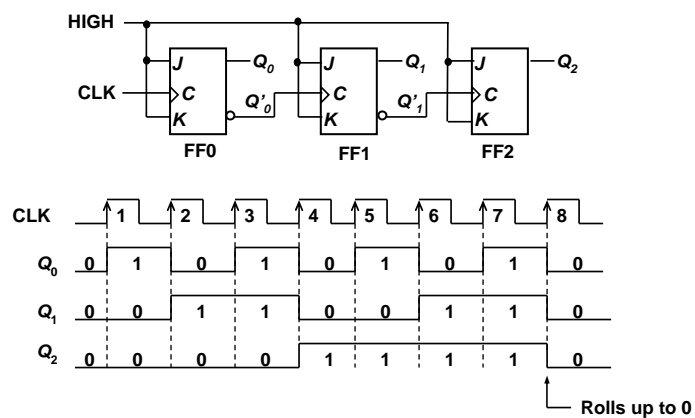

Lecture 9: Flip-Flops and Registers

32

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.




The diagram shows four clock cycles. In each cycle, the output of one flip-flop becomes the input of the next. The timing parameters are defined as follows:

- $t_{PLH}$  (CLK to  $Q_0$ ): Propagation delay from the clock edge to the output  $Q_0$ .
- $t_{PHL}$  ( $Q_0$  to  $Q_1$ ): Propagation delay from the output  $Q_0$  to the input of the next flip-flop.
- $t_{PHL}$  ( $Q_0$  to  $Q_1$ ): Propagation delay from the output  $Q_0$  to the input of the next flip-flop.
- $t_{PLH}$  ( $Q_1$  to  $Q_2$ ): Propagation delay from the output  $Q_1$  to the input of the next flip-flop.

- ## Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

 
[illegible]

## Lecture 9: Flip-Flops and Registers

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## BCD Ripple Counter

- BCD Counters are counters with 10 states. In a BCD ripple counter we need to detect  $(1010)_2$  in order to reset the counter


 


Lecture 9: Flip-Flops and Registers

35

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## BCD Ripple Counter

  



Lecture 9: Flip-Flops and Registers

36

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Ripple Down Counters

- A ripple counter can be made to count down by changing the source for the next FF from Q to Q':

  


Lecture 9: Flip-Flops and Registers

37

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Cascading Ripple Counters

- It possible to implement large ripple counters by cascading smaller ripple counters.
- Example: A 5-bit ripple counter constructed from a 2-bit counter and a 3-bit counter:

 


Lecture 9: Flip-Flops and Registers

38

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Cascading Ripple Counters

- A two digit BCD counter:

 

Lecture 9: Flip-Flops and Registers

39

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Example: Ripple Counters in VHDL.

- For this example I'll use the 50 MHz oscillator in the DE0-CV board to make a BCD seconds counter (0 to 59) and display the current count using the 7-segment displays.
- The 50 MHz clock signal is attached to pin\_N2.

Lecture 9: Flip-Flops and Registers

40

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## VHDL BCD Counter

```
LIBRARY ieee;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.STD_LOGIC_ARITH.all;
USE IEEE.STD_LOGIC_UNSIGNED.all;

ENTITY BCDCOUNT IS
    port(
        KEY0, CLK_50      :IN      STD_LOGIC;
        MSD, LSD :OUT STD_LOGIC_VECTOR (0 to 6)
    );
END BCDCOUNT;

ARCHITECTURE a of BCDCOUNT is
    SIGNAL ClkFlag: STD_LOGIC;
    SIGNAL Internal_Count: STD_LOGIC_VECTOR(28 downto 0);
    SIGNAL HighDigit, LowDigit: STD_LOGIC_VECTOR(3 downto 0);
    SIGNAL MSD_7SEG, LSD_7SEG: STD_LOGIC_VECTOR(0 to 6);

BEGIN

    LSD<=LSD_7SEG;
    MSD<=MSD_7SEG;
```

Lecture 9: Flip-Flops and Registers

41

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Divide the 50MHz to get 0.5Hz

```
PROCESS(CLK_50)
BEGIN
    if(CLK_50'event and CLK_50='1') then
        if Internal_Count<25000000 then
            Internal_Count<=Internal_Count+1;
        else
            Internal_Count<=(others => '0');
            ClkFlag<=not ClkFlag;
        end if;
    end if;
END PROCESS;
```

Lecture 9: Flip-Flops and Registers

42

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Two BCD Counters. The output on one is the clock of the other...

```
PROCESS(ClkFlag, KEY0)
BEGIN
    if(KEY0='0') then -- reset
        LowDigit<="0000";
        HighDigit<="0000";
    elsif(ClkFlag'event and ClkFlag='1') then
        if (LowDigit=9) then
            LowDigit<="0000";
            if (HighDigit=5) then
                HighDigit<="0000";
            else HighDigit<=HighDigit+'1';
            end if;
        else
            LowDigit<=LowDigit+'1';
        end if;
    end if;
END PROCESS;
```

Lecture 9: Flip-Flops and Registers

43

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## BCD to 7-segment

```
PROCESS(LowDigit, HighDigit)
BEGIN
    case LowDigit is
        when "0000" => LSD_7SEG <= "0000001";
        when "0001" => LSD_7SEG <= "1001111";
        when "0010" => LSD_7SEG <= "0010010";
        when "0011" => LSD_7SEG <= "0000110";
        when "0100" => LSD_7SEG <= "1001100";
        when "0101" => LSD_7SEG <= "0100100";
        when "0110" => LSD_7SEG <= "0100000";
        when "0111" => LSD_7SEG <= "0001111";
        when "1000" => LSD_7SEG <= "0000000";
        when "1001" => LSD_7SEG <= "0000100";
        when others => LSD_7SEG <= "1111111";
    end case;

```

Lecture 9: Flip-Flops and Registers

44

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

# BCD to 7-segment

```

case HighDigit is
    when "0000" => MSD_7SEG <= "0000001";
    when "0001" => MSD_7SEG <= "1001111";
    when "0010" => MSD_7SEG <= "0010010";
    when "0011" => MSD_7SEG <= "0000110";
    when "0100" => MSD_7SEG <= "1001100";
    when "0101" => MSD_7SEG <= "0100100";
    when "0110" => MSD_7SEG <= "0100000";
    when "0111" => MSD_7SEG <= "0001111";
    when "1000" => MSD_7SEG <= "0000000";
    when "1001" => MSD_7SEG <= "0000100";
    when others => MSD_7SEG <= "1111111";
end case;
END PROCESS;

end a;


```

Lecture 9: Flip-Flops and Registers

45

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## BCD Ripple Connection Using Multisim

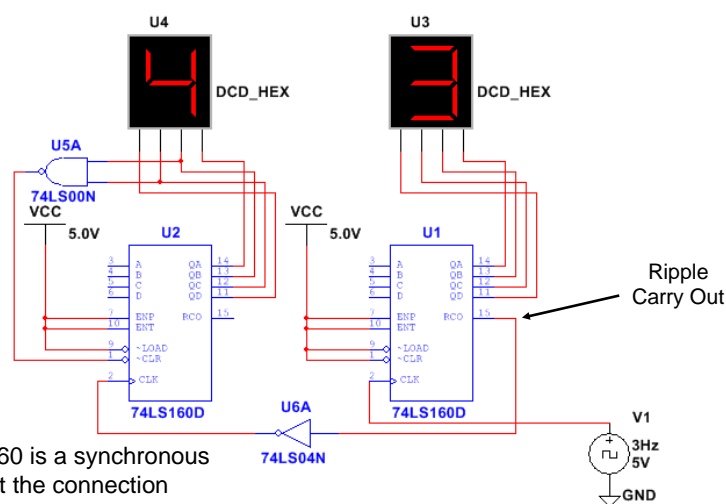


The 74LS160 is a synchronous counter, but the connection between both is asynchronous.

Lecture 9: Flip-Flops and Registers

46

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## BCD Ripple Connection Using Multisim

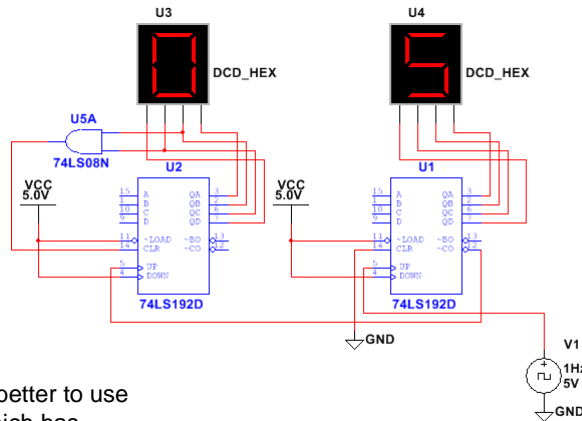

For the lab is better to use a 74LS192 which has asynchronous load and reset inputs.

Lecture 9: Flip-Flops and Registers

47

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## Exercises

- Design a BCD ripple counter using Flip-Flops that follows the sequence 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 1, 2, 3, etc. (You can use it for lab 3)
- Design a 2-digit BCD down counter.

Lecture 9: Flip-Flops and Registers

48

Copyright © 2009-2016, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.