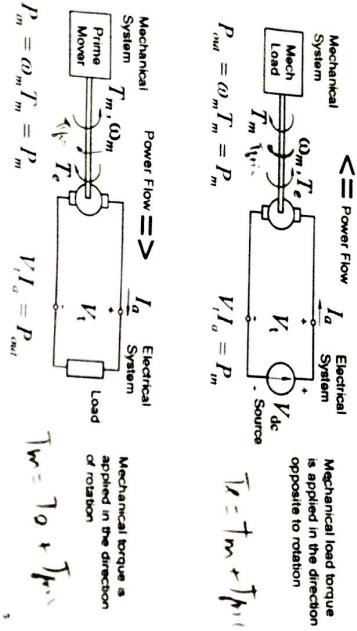



DC Machine Motoring and Generating

F.I.C. 2013-2014



- Current-carrying conductor in magnetic field
=> mechanical force

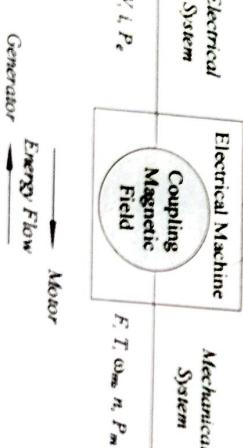
- Conductor moves in magnetic field
=> voltage induced, emf



6

Consider a conductor frame (single-coil)
Force & Torque

F.I.C. 2013-2014

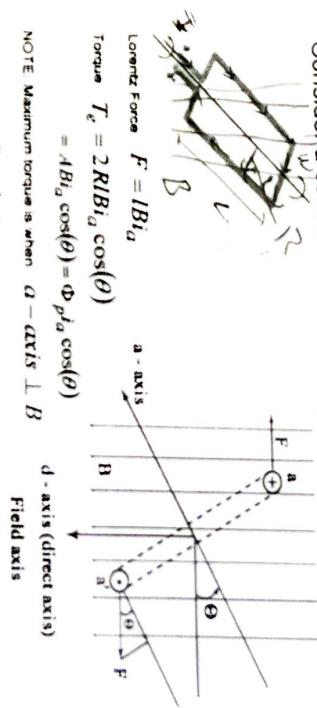

Induced Voltage
Consider a conductor frame (single-coil)

Faraday's Law: $e = \frac{d\Phi}{dt}$

$\Phi = BA \sin(\theta) = BA \sin(\omega t)$


$\Phi = BA \sin(\omega t) = \Phi_p \sin(\omega t)$

$e = \frac{d\Phi}{dt} = \omega \Phi_p \cos(\omega t) \Rightarrow e \sim \omega \Phi_p$

8


Conductor Frame (1-turn coil)

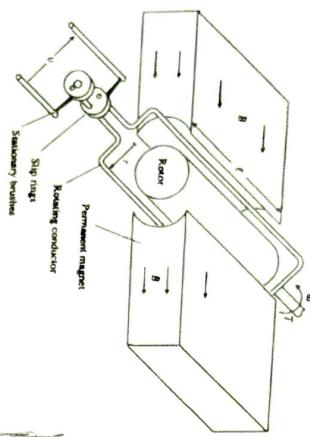Consider a conductor frame placed on a rotor between magnetic poles



Elementary DC Machine

Consider a two-pole case

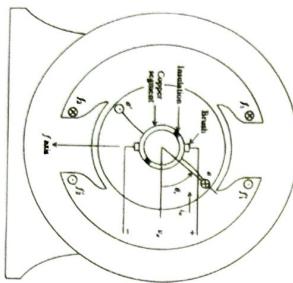

ELEC 343 S.19 W3

Voltage Equations

$$v_f = r_f i_f + \frac{dI_f}{dt}$$

$$v_a = r_a i_a + \frac{d\lambda_a}{dt}$$

Flux linkages

$$\lambda_f = L_{ff} i_f + L_{fa} i_a$$

$$\lambda_a = L_{af} i_a + L_{aa} i_f$$

Approximate the mutual inductance $L_{af} = L_{fa} = -L \cos(\theta_r)$

10

More Realistic DC Machine

ELEC 343 S.19 W3

Resulted Winding Connection



$$e_a = \omega_r L_i \sin(\theta_r)$$

$$v_a = r_a i_a + \frac{d\lambda_a}{dt}$$

Assume

$$i_a = 0 \text{ and } \theta_r = \omega_r t$$


$$\lambda_a = L_a i_a + L_{af} i_f$$

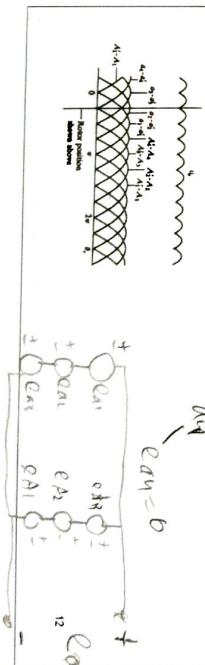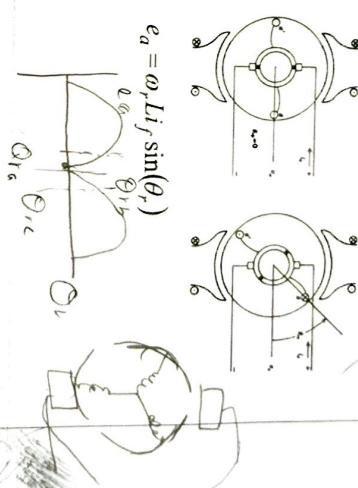

More Realistic DC Machine

ELEC 343 S.19 W3


Resulted Winding Connection

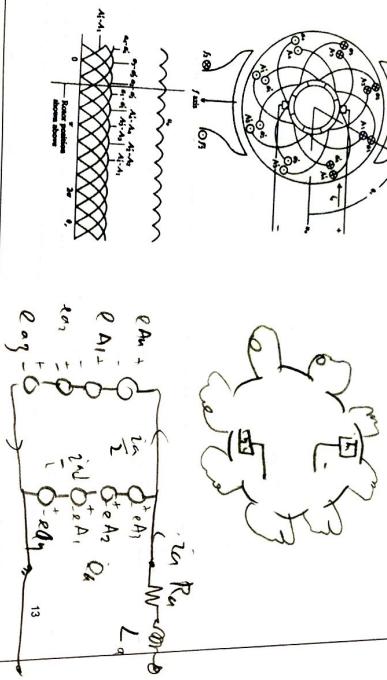


DC Machine Construction

ELEC 343 S.19 W3

Permanent Magnet (PM) DC machine

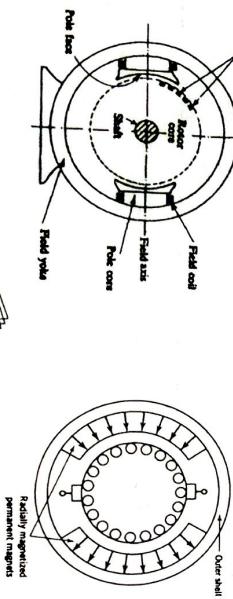


Rotor construction

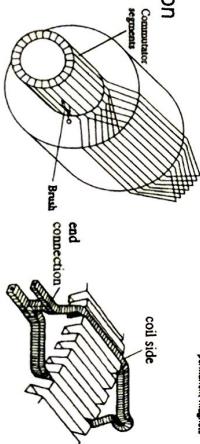

14

Cutaway View of a Two-Pole DC Machine


ELEC 343 S.19 W3

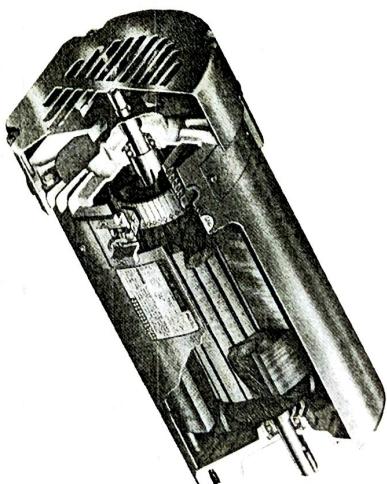

15

Equivalent Circuit

ELEC 343 S.19 W3

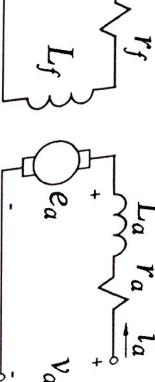

V_f - is the field voltage
 i_f - is the field current
 r_f - field winding resistance
 L_f - field winding inductance
 V_a - applied terminal voltage
 i_a - is the armature current
 L_a - armature winding inductance
 r_a - armature winding + brush resistance
 e_a - induced back emf (voltage)

16

Dynamic Equivalent Circuit

ELEC 343 S.19 M.3

Field Winding Equations

$$v_f = r_f i_f + \frac{d\lambda_f}{dt}$$

$$\lambda_f = N_f \Phi_p = L_f i_f$$

$$e_a = k_1 \omega_r \Phi_p$$

$$\text{Electromagnetic Torque } T_e = k_2 \Phi_p i_a$$

$$\text{Power balance } T_e \omega_r = k_2 \Phi_p i_a \omega_r = e_a i_a = k_1 \omega_r \Phi_p i_a$$

$$P_e = T_e \omega_r = e_a \cdot i_a = \text{consuming power}$$

$$k_1 = k_2 = K \text{ machine Design constant}$$

17

Equivalent Circuit

ELEC 343 S.19 M.3

$$\text{Recall flux } \Phi_p = \frac{\lambda_f}{N_f} = \frac{L_f}{N_f} I_f \quad \text{Torque}$$

$$e_a = k \Phi_p \omega_r = k \frac{L_f}{N_f} i_f \omega_r \quad T_e = k \Phi_p i_a = k \frac{L_f}{N_f} i_f i_a$$

$$\text{Define } L_{af} = k \frac{L_f}{N_f} \quad \begin{matrix} \text{- is the mutual inductance} \\ \text{between field and rotating} \\ \text{armature winding} \end{matrix} \quad L_{af} = \frac{N_a N_f}{\mathfrak{R}}$$

Re-define expression for back emf and torque

$$e_a = L_{af} i_f \omega_r = k_v \omega_r \quad T_e = L_{af} i_f i_a = k_i i_a$$


$$\text{Machine voltage/torque constant for PM machine} \quad k_v = k_i = L_{af} i_f$$

18

Steady-State

ELEC 343 S.19 M.3

Field Winding Equations

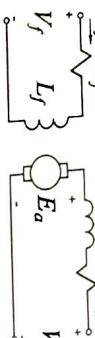

Field Winding Equations

$$V_f = R_f I_f$$

$$\lambda_f = N_f \Phi_p = L_f I_f$$


$$\text{Electromagnetic torque } T_e = L_{af} I_f I_a = k_t I_a$$

$$\text{Torque balance } T_e = T_m + T_{\text{mech_loss}}$$

19

Example 1: No Load Test PM Motor

ELEC 343 S.19 M.3

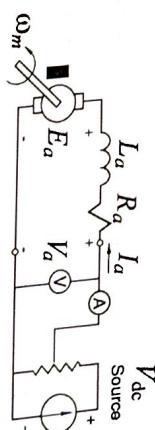

Assume you know R_a
Measure I_a, V_a, ω_r

Armature Equations

$$V_a = R_a I_a + E_a$$

$$E_a = I_a E_a = \omega_r T_e$$

$$T_e = T_{\text{friction}} = \omega_r D_m$$

20

$$\begin{aligned} T_e &= k_v I_a \\ E_a &= k_v \omega_r \\ k_t &= k_v \quad \begin{matrix} \text{Torque / voltage} \\ \text{machine constant} \end{matrix} \end{aligned}$$

20

Example 2: PM DC Motor

ELEC 343 S 19 W3

Consider a small PM DC Motor with the following parameters:
 $V_{\text{out}} = 6V$, $I_{\text{no load}} = 0.15A$, $R = 7\Omega$, and torque constant $K_t = 0.014 \text{ Nm/Arad}$
 Find no-load speed $n_{\text{no load}}$, back emf E_b , and friction torque T_{friction} at $V_i = 6V$

$$V_t = R_a I_a + E_b = R_a I_a + K_t \cdot \omega$$

$$\omega_{\text{no load}} = \frac{V_t - R_a I_a}{K_t} = \frac{6 - 7 \cdot 0.15}{0.014} = 353.57 \text{ rad/sec}$$

$$n_{\text{no load}} = \frac{30}{\pi} \omega_{\text{no load}} = 3535.7 \text{ rpm}$$

$$\text{Back emf}, E_b = K_t \omega = 0.014 \cdot 353.57 = 49.5V$$

$$E_b \text{ corresponds to freq } \omega$$

$$T_{\text{no load}} = K_t \cdot I_a = 0.014 \cdot 0.15 = 0.0021 \text{ N.m}$$

$$T_{\text{no load}} = \frac{P_e}{\omega} = \frac{I_a E_b}{\omega} = \frac{0.15 \cdot 49.5}{353.57} = 0.0021 \text{ N.m}$$


$$T_{\text{no load}} = T_e = 0.0021 \text{ N.m}$$

21

Basic Types of DC Machines

ELEC 343 S 19 W3

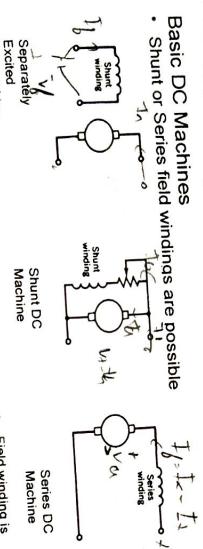- Basic DC Machines, Shunt or Series field windings are possible




- Field winding is designed for up to rated armature voltage
 - Field winding has large number of turns
 - Field current is the same as the armature current compared to armature current
- 22

Basic Types of DC Machines

ELEC 343 S 19 W3

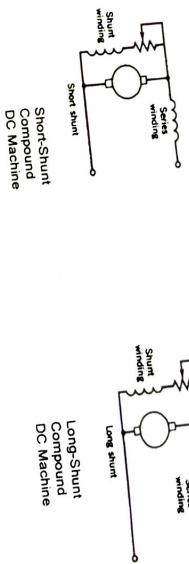- Both Shunt and Series field windings are present




23

Parameters of DC Machine

ELEC 343 S 19 W3

Locked-Rotor Test (DC Measurements)

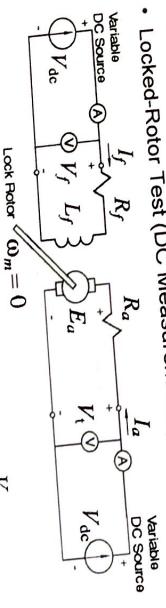

$$R_f = \frac{V_f}{I_f}$$


$$R_a = \frac{V_a}{I_a}$$

(armature + brush combined resistance at no speed)

24

Parameters of DC Machine

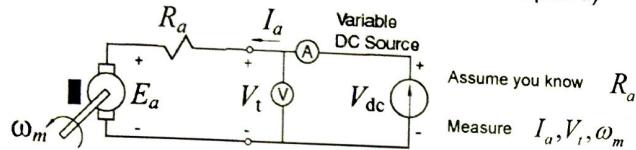- No Load Test for PM Motors (Friction vs. Speed)



$$V_t = R_a I_a + E_a$$

$$T_e = K_a \Phi_p I_a = K_t I_a$$

$$E_a = K_a \Phi_p \omega_m = K_v \omega_m$$


$K_t = K_v$ Torque / voltage
machine constant

$$k_f = k_r = \frac{V_t - R_a I_a}{\omega_m}$$

$$P_e = I_a E_a = \omega_m T_e$$

$$T_e = T_{fric}(\omega_m) = \omega_m D_m$$

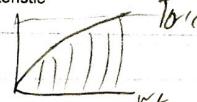
Measure Friction Torque-Speed
Characteristic



25

Parameters of DC Machine

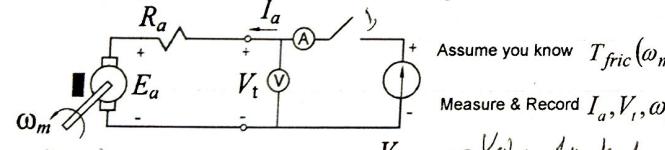- Stopping Transient for Determining Inertia




$$T_e = T_m + T_{fric}(\omega_m) + J \frac{d\omega_m}{dt}$$

$$E_a = K_a \Phi_p \omega_m = K_v \omega_m$$

$$T_{fric}(\omega_m) = -J \frac{\Delta \omega_m}{\Delta t} = -J \frac{\Delta E_a}{K_v \Delta t}$$

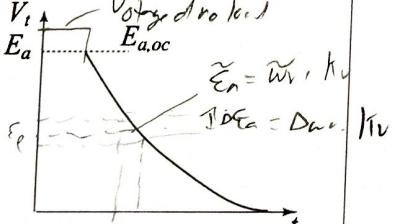
$$J = \frac{T_m(w_r) - k_v D_f}{D_f \epsilon_r}$$




26

Parameters of DC Machine

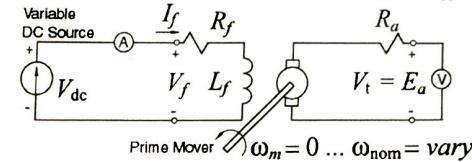- Open-Circuit Test (Generated Voltage vs. Speed)



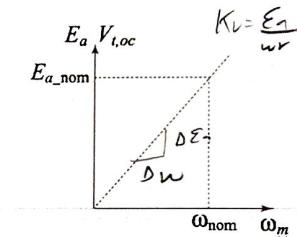
$$E_a = K_a \Phi_p \omega_m = K_a \frac{L_f}{N_f} I_f \omega_m = L_{af} I_f \omega_m$$



ELEC 343, S-19 M-3


Parameters of DC Machine

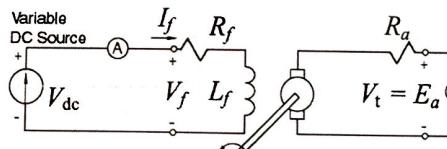- Open-Circuit Test (Generated Voltage vs. Field Currents)



$$\Phi_p = \frac{\lambda_f}{N_f} = \frac{L_f}{N_f} I_f$$

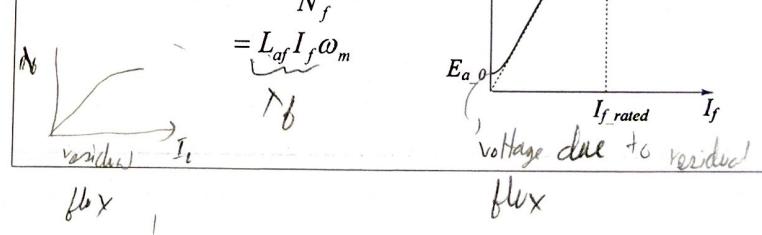
$$E_a = K_a \Phi_p \omega_m = K_a \frac{L_f}{N_f} I_f \omega_m = L_{af} I_f \omega_m$$




ELEC 343, S-19 M-3

DC Machines Characteristics:


Speed Regulation (for Motors)

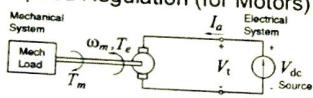

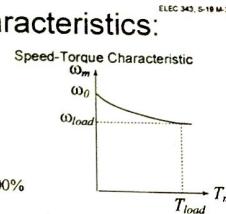
$$SR = \frac{\omega_{m,no_load} - \omega_{m,load}}{\omega_{m,load}} \cdot 100\% = \frac{n_{no_load} - n_{load}}{n_{load}} \cdot 100\%$$



Voltage Regulation (for Generators)

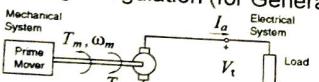

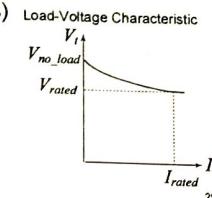
$$VR = \frac{V_{t,no} - V_{t,load}}{V_{t,load}} \cdot 100\% = \frac{V_{no_load} - V_{nom}}{V_{nom}} \cdot 100\%$$



Separately Excited

Field Winding Equations

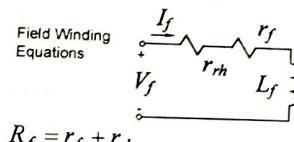

$$R_f = r_f + r_{rh}$$

$$V_f = R_f I_f$$

$$\lambda_f = N_f \Phi_p = L_f I_f$$

$$\text{Electromagnetic torque } T_e = L_{af} I_f I_a$$

Torque balance

$$T_e = T_m + T_{mech_loss}$$

ELEC 343, S-19 M-3


Armature Equations

$$V_a = r_a I_a + E_a$$

$$E_a = \omega_r L_{af} i_f$$

30


Separately-Excited DC Motor

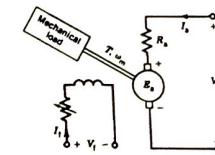

$$V_a = R_a I_a + E_a$$

$$E_a = L_{af} I_f \omega_r$$

$$T = L_{af} I_f I_a$$

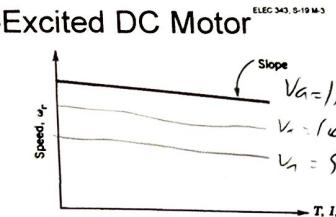


$$\omega_r = \frac{E_a}{L_{af} I_f} = \frac{V_a - I_a R_a}{L_{af} I_f}$$

$$\omega_r = \left(\frac{V_a}{L_{af} I_f} \right) \left(\frac{R_a}{(L_{af} I_f)^2} \right) T$$

hanging load
Wye

Shunt DC Motor

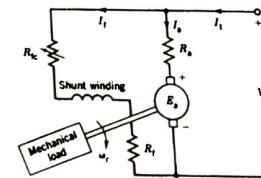

$$\omega_r = \frac{V_a}{L_{af} I_f} - \frac{R_a}{(L_{af} I_f)^2} T$$


$$L_{af} I_f = \frac{L_{af} V_a}{R_f + R_s}$$





$$\omega_r = \frac{R_f, total}{L_{af}} - \frac{R_a R_f, total}{(L_{af} V_a)^2} T$$

No load
slope

speed
slope

32

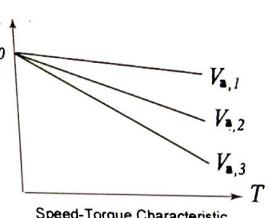

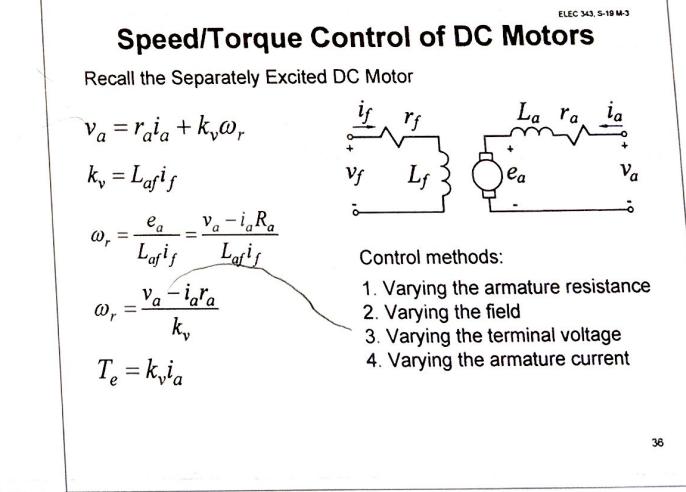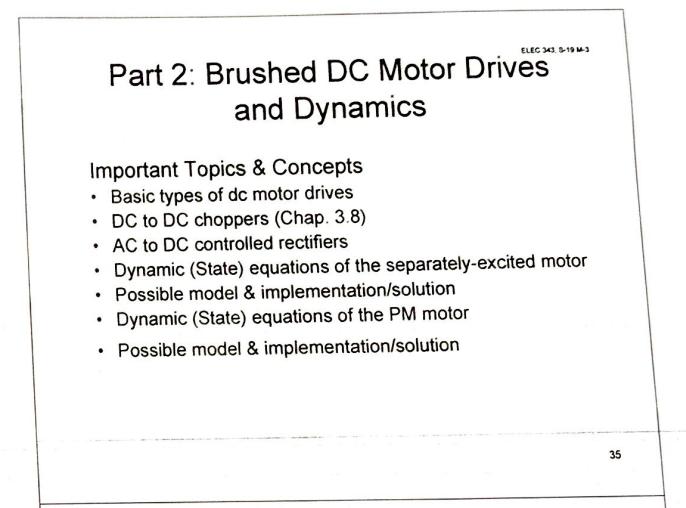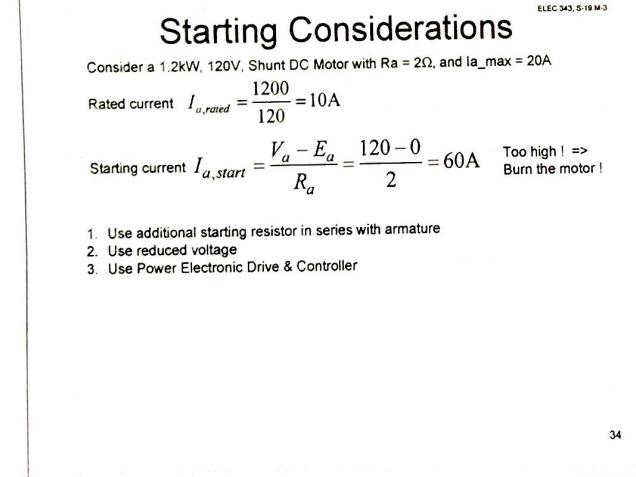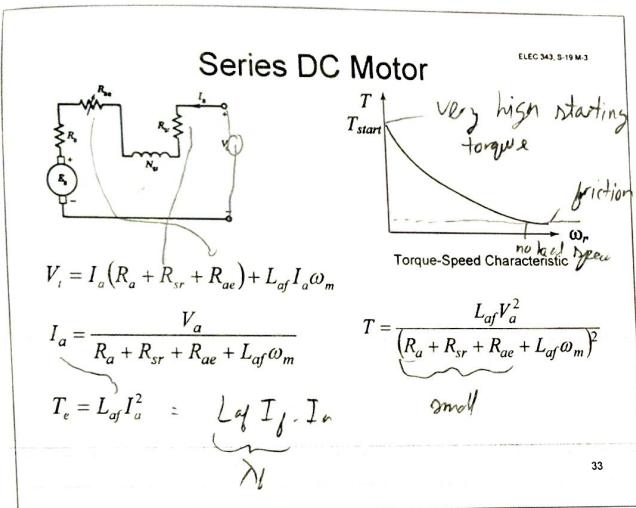

Solid-State Converters for DC Motors

- DC-DC Converters (Choppers) – used with small & large motors
- Voltage Source (VS) (Pulse Width Modulation – PWM)
 - One-quadrant
 - Two-quadrant
 - Four-quadrant
 - Current Source (CS) (Hysteresis & Delta Modulation)
 - One-quadrant
 - Two-quadrant
 - Four-quadrant
-


AC-DC Controlled Rectifiers – used with large motors

- Single-Phase
 - Half-wave
 - Full bridge (full wave)
- Three-Phase
 - Half-wave
 - Full bridge (full wave)

37


DC-DC Converters (Choppers)

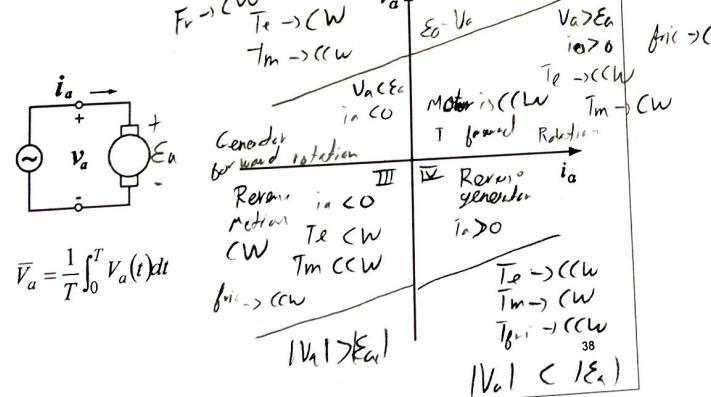Assume a dc voltage source wherein the averaged output voltage can be controlled



38

One-Quadrant VS DC-DC Converter

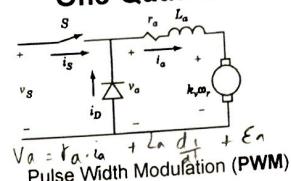

Pulse Width Modulation (PWM)

$d = t_1 / T$


duty cycle

$\bar{V}_a = \frac{1}{T} \int_0^T v_a(t) dt = \frac{t_1}{t_1 + t_2} V_s$

39

- Switch can be realized using:
- Bipolar Junction Transistor (BJT)
 - Insulated Gate Bipolar Transistor (IGBT)
 - Metal Oxide Semiconductor Field Effect Transistor (MOSFET)

Two-Quadrant VS DC-DC Converter

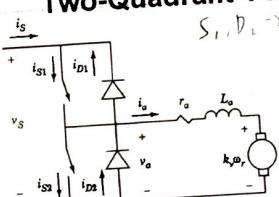

Pulse Width Modulation (PWM)


$V_a = d * V_s$

$$d = \frac{t_1}{t_1 + t_2} = \frac{I_1}{T}$$

40

H-bridge converter

Four-Quadrant VS DC-DC Converter

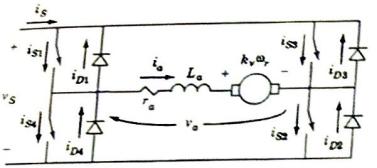

ELEC 343, S-19 M-3

Pulse Width Modulation (PWM)

$$\bar{v}_a = \frac{1}{T} \int_0^T v_a(t) dt = dV_s = 2(d - \frac{1}{2})V_s$$

$$0 < d \leq 1$$

$$-V_s < V_a < +V_s$$


41

ELEC 343, S-19 M-3

Thyristor Controlled Rectifiers

Control the Averaged Output Voltage

a) Single-phase, half-wave

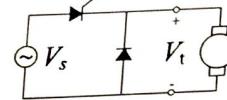


$$V_s = \sqrt{2}V_{rms} \sin(\omega t)$$

$$\bar{V}_t = \frac{1}{T} \int_0^T V_t(t) dt = \frac{V_{rms}}{\sqrt{2}\pi} (1 + \cos(\alpha))$$

$$0 \leq \alpha \leq \pi$$
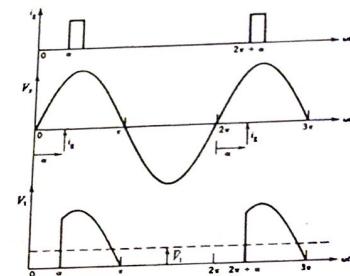
$$0 \leq \bar{V}_t \leq \frac{\sqrt{2}}{\pi} V_{rms}$$





43

ELEC 343, S-19 M-3

Thyristor Controlled Rectifiers

Control the Averaged Output Voltage

b) Single-phase, full-wave

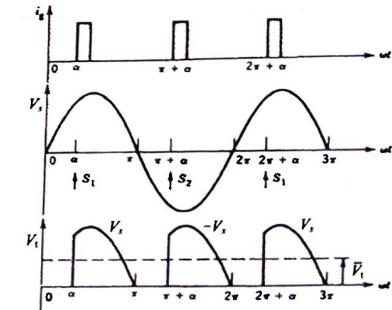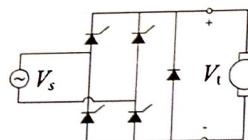

$$V_s = \sqrt{2}V_{rms} \sin(\omega t)$$

$$\bar{V}_t = \frac{1}{T} \int_0^T V_t(t) dt = \frac{\sqrt{2}V_{rms}}{\pi} (1 + \cos(\alpha))$$

$$0 \leq \alpha \leq \pi$$


$$0 \leq \bar{V}_t \leq \frac{2\sqrt{2}}{\pi} V_{rms}$$

44

Current Source DC-DC Converter

ELEC 343, S-19 M-3

Hysteresis Modulation (HM)

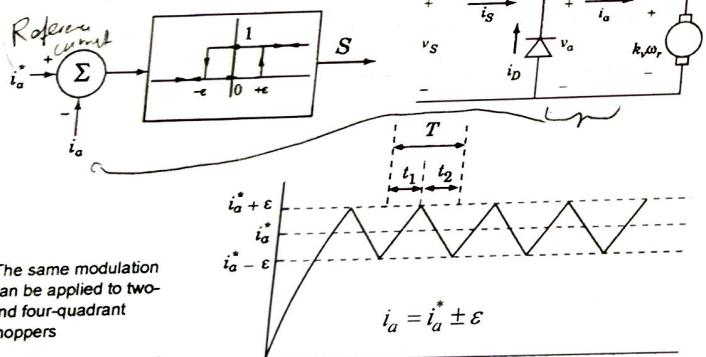

The same modulation can be applied to two- and four-quadrant choppers

$$T_d = K_d \cdot i_a$$

42


Thyristor Controlled Rectifiers

Control the Averaged Output Voltage
d) Three-phase, full-wave

$$V_A = \sqrt{2}V_{rms} \sin(\omega t)$$

$$V_B = \sqrt{2}V_{rms} \sin(\omega t - 120^\circ)$$
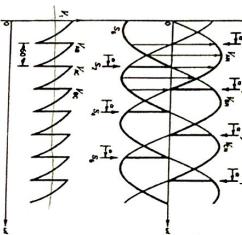
$$V_C = \sqrt{2}V_{rms} \sin(\omega t + 120^\circ)$$



$$\bar{V}_r = \frac{1}{T} \int_0^T V_r(t) dt \quad 0 \leq \alpha \leq \pi$$


$$0 \leq \bar{V}_r \leq \frac{3\sqrt{6}}{\pi} V_{rms}$$

45

Closed-Loop Electric Drive System

ELEC 343 S19 M3


Mechanical
System

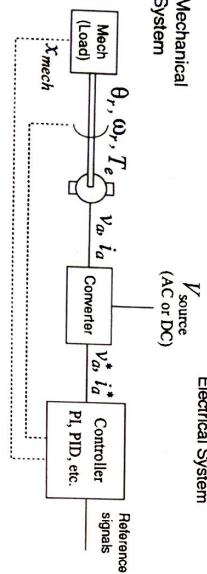

Dynamic models are needed for analyzing and designing complex electro-mechanical systems!

Dynamic Modeling

Circuit is valid for
transient analysis

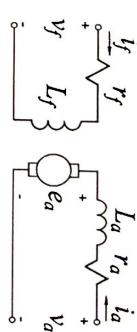

Coupling Terms
 $e_a = \omega_r L_g i_f$

$T_e = L_g i_f i_a$

$$v_f = r_f i_f + \frac{di_f}{dt} = r_f i_f + L_f \frac{di_a}{dt}$$

$$v_a = r_a i_a + \frac{di_a}{dt}$$

Speed Equation

$$T_e = J \frac{d\omega_r}{dt} + T_m + D_m \omega_r$$

much on in! pulley, etc.

47

Re-Write the Equations to Express Derivatives

State Equations *(The Nyaan of ODE)*

$$\left\{ \begin{array}{l} \frac{di_a}{dt} = -\frac{r_a}{L_a} i_a - \frac{1}{L_a} e_a + \frac{1}{L_a} v_a \\ \frac{di_f}{dt} = -\frac{r_f}{L_f} i_f + \frac{1}{L_f} v_f \end{array} \right.$$

$$e_a = \omega_r L_g i_f$$

$$T_e = L_g i_f i_a$$

product
hor. line

$$\frac{d\omega_r}{dt} = -\frac{D_m}{J} \omega_r + \frac{1}{J} (T_e - T_m)$$

Are these equations coupled or decoupled?
Are these equations linear or non-linear?

How do we solve these equations?


M.J.L. / nimekay

48

Implementation of State Equations

$$\frac{di_a}{dt} = -\frac{r_a}{L_a} i_a - \frac{1}{L_a} v_a + \frac{1}{L_a} v_d$$
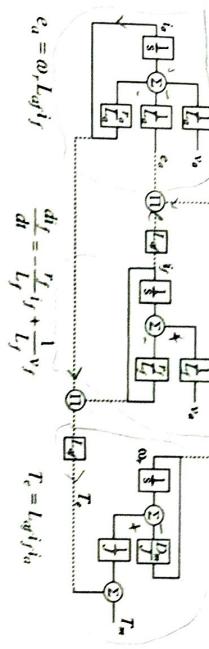
$$\frac{dv_d}{dt} = -\frac{D_m}{J} \omega_r + \frac{1}{J} (T_e - T_m)$$



$$v_d = \omega_r L_{af} i_f$$

$$\frac{di_f}{dt} = -\frac{r_f}{L_f} i_f + \frac{1}{L_f} v_f$$

$$T_e = L_{af} i_f i_a$$

Try to implement it in Simulink?

Is this a unique implementation?

49

Implementation of State Equations

Re-write the equations

$$i_a = \frac{v_d - r_a i_a}{L_a}$$

$$v_f = r_f (1 + r_f s) i_f$$

$$v_d = r_a (1 + \tau_a s) i_a + c_a$$

$$\omega_r = \omega_r L_{af} i_f$$

$$T_e = T_m + (D_m + J_S) \omega_r$$

$$T_e = L_{af} i_f i_a$$

Define time constants


$$\tau_a = \frac{L_a}{r_a}$$

$$\tau_f = \frac{L_f}{r_f}$$

$$\tau_a = \frac{1}{(r_a L_a s)} \quad \text{and} \quad \tau_f = \frac{1}{(r_f L_f s)}$$

$$S = \frac{\log L_a}{\sqrt{L_a}}$$

5-HP Shunt DC Motor Simulink Model

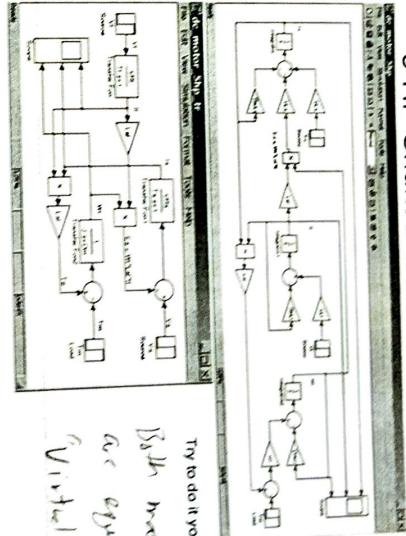


50

Dynamic Response of a 5-HP DC Motor

Motor parameters:
 $V_a \approx 240V$, $R_f = 240\Omega$, $L_f = 120H$, $R_a = 0.6\Omega$, $L_a = 0.012H$, $\omega_{at} = 1800$,
 $J = 1kg \cdot m^2$, $D_m = 16.4 N \cdot m \cdot s$, $T_m = 29.2 N \cdot m$

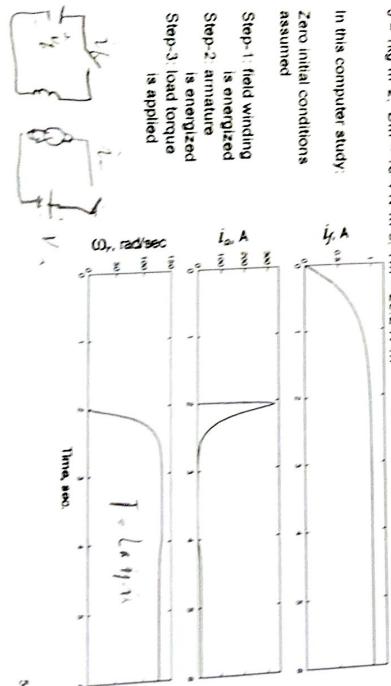In this computer study:
Zero initial conditions assumed
Step-1: field winding is energized
Step-2: armature is energized
Step-3: load torque is applied



51

PM DC Motor Dynamics

Lec 3.5.2.10.2

$$\begin{aligned} \text{State Equations} \\ \frac{di_a}{dt} &= -\frac{r_a}{L_a} i_a - \frac{1}{L_a} e_a + \frac{1}{L_a} v_a \\ \frac{d\omega_r}{dt} &= -\frac{D_m}{J} \omega_r + \frac{1}{J} (T_e - T_m) \end{aligned}$$

Are these equations coupled or decoupled?
How do we solve these equations?

$$\begin{aligned} \text{Standard State-Space Form} \\ \frac{d}{dt} \begin{bmatrix} i_a \\ \omega_r \end{bmatrix} &= \begin{bmatrix} -\frac{r_a}{L_a} & -\frac{k_v}{L_a} \\ \frac{1}{L_a} & -\frac{D_m}{J} \end{bmatrix} \begin{bmatrix} i_a \\ \omega_r \end{bmatrix} + \begin{bmatrix} \frac{1}{L_a} \\ -\frac{1}{J} \end{bmatrix} \begin{bmatrix} v_a \\ T_m \end{bmatrix} \end{aligned}$$

$$\begin{aligned} L \text{ (load)} & \quad T_m \text{ (in variation)} \\ CL \quad T_i & \quad \frac{dx}{dt} = Ax + Bu \end{aligned}$$



Electrical mechanical model

PM DC Motor Implementations

Lec 3.5.2.10.2

$$\begin{aligned} \text{State Equations} \\ \frac{di_a}{dt} &= -\frac{r_a}{L_a} i_a - \frac{1}{L_a} e_a + \frac{1}{L_a} v_a \\ \frac{d\omega_r}{dt} &= -\frac{D_m}{J} \omega_r + \frac{1}{J} (T_e - T_m) \end{aligned}$$

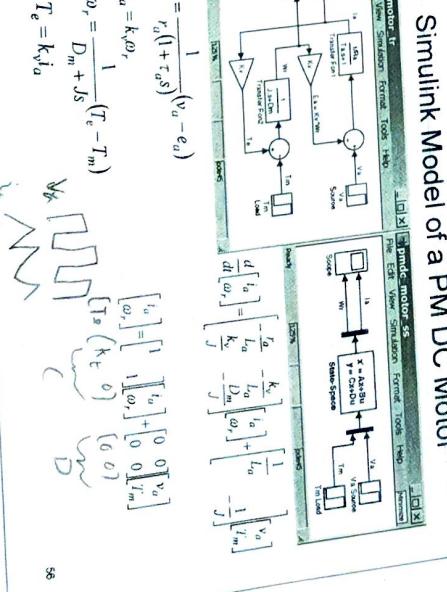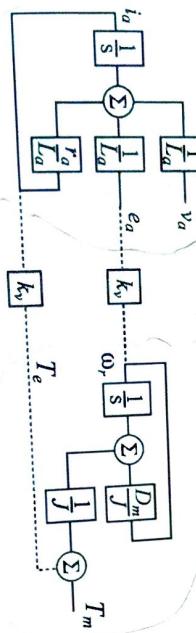Are these equations coupled or decoupled?
Are these equations linear or non-linear?
How do we solve these equations?



Implementation of State Equations

Lec 3.5.2.10.2

$$\begin{aligned} \text{Re-write the equations} \\ v_a &= r_a (1 + \tau_a s) i_a + e_a \\ e_a &= k_v \omega_r \\ T_e - T_m &= (D_m + J s) \omega_r \\ T_e &= k_v i_a \end{aligned}$$

Define time constants


$$\tau_a = \frac{L_a}{r_a} \quad \tau_f = \frac{L_f}{r_f}$$

$$i_a = \frac{1}{(J s + D_m)} (v_a - \omega_r)$$

$$\omega_r = \frac{1}{(J s + D_m)} (T_f - T_m)$$

Simulink Model of a PM DC Motor

Lec 3.5.2.10.2

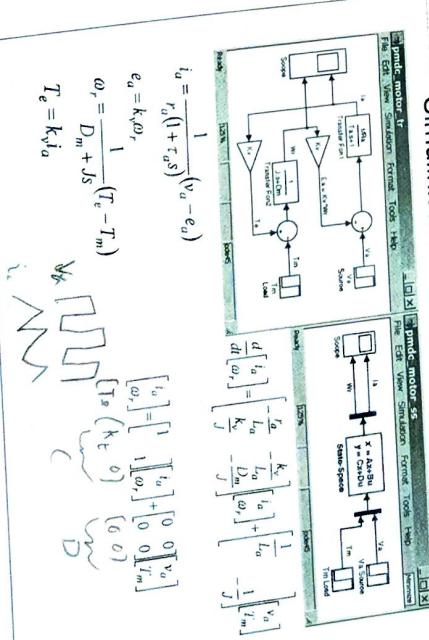

54

Lec 3.5.2.10.2

55

56

Dynamic Response of a 6V PM DC Motor

ELEC 343, § 19.4.3

Motor parameters:


$V_a = 6V$, $R_a = 7\Omega$, $L_a = 120mH$, $K_v = 0.0141 N \cdot A/m$, $J = 1.08e-6 kg \cdot m^2$,

$D_m = 6.01e-6 N \cdot m \cdot s$, $T_m = 3.53e-3 N \cdot m$


In this computer study:

Zero initial conditions assumed

Step-1: voltage is applied

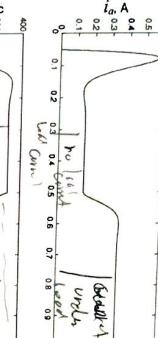

Step-2: load torque is applied

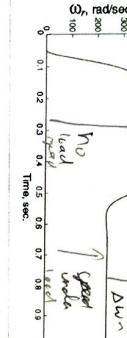

57