



University of British Columbia
Electrical and Computer Engineering
Digital Design and Microcomputers CPEN312

L05: Reduction Techniques.

Dr. Jesús Calviño-Fraga. P.Eng.
Department of Electrical and Computer Engineering, UBC
Office: KAIS 3024
E-mail: jesusc@ece.ubc.ca
Phone: (604)-827-5387

January 11/16, 2019

Copyright © 2009-2019, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Objectives

- Boolean function reduction using K-maps
- Product of Maxterms/Sums POS simplification with K-maps
- “Don’t Care” uses in simplification
- Fundamental gates: NAND & NOR

L05: Reduction Techniques

2

Copyright © 2009-2019, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Reduction via Geometry

- Recall this reduction trick:
 - $Y = A.B + A.B' = A.(B+B') = A$
 - $X = A'.B + A.B = B.(A+A') = B$
- Finding these $(A+A')$ can be easily achieved with a map.
- For Boolean functions we use Karnaugh maps or K-maps.
- I have seen it working for 2 to 6 variables.


L05: Reduction Techniques

3

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Karnaugh Maps

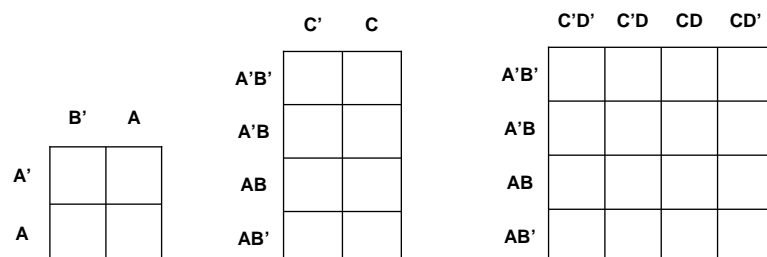- The idea is to arrange the truth table into a square grid where each cell corresponds to a truth table row. They look like this:




Two, three, and four variable Karnaugh maps.

L05: Reduction Techniques

4

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Karnaugh Maps

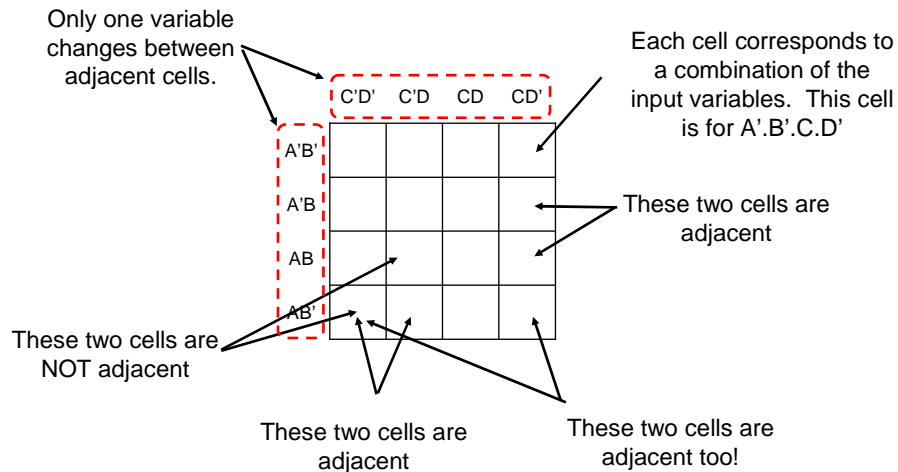

L05: Reduction Techniques

5

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Using K-Maps

- ONLY one variable changes when moving from adjacent cells. That is why we arrange the rows/columns as $A'B'$, $A'B$, AB , AB'
- You can arrange the cells in any order, but the rule above must hold. $A'B$, AB , AB' , $A'B'$ will work also.
- Each cell represents a minterm.

L05: Reduction Techniques

6

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Using K-Maps

- How this works? Consider the truth table below and its K-map.

In			Out
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

	c'	c
A'B'	1	1
A'B	1	0
AB	0	0
AB'	0	0

Every output in the truth table corresponds to a cell in the K-map

L05: Reduction Techniques

7

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Using K-Maps

- Now look at the ones in the K-map and encircle them together with all adjacent cells. The oval must contain only 1, 2, 4, 8, 16, etc. ones. An oval of 5 ones, for example, is not valid!

	c'	c
A'B'	1	1
A'B	1	0
AB	0	0
AB'	0	0

Now look at what variables remain constant within each encircle.

The final answer is the sum of the equation for each encircle:

$$X = A'B' + A'C'$$

L05: Reduction Techniques

8

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Verify the Answer with Algebra...

In			Out
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$X = A'.B'.C' + A'.B'.C + A'.B.C'$$

$$X = A'.B'.(C+C') + A'.B.C'$$

$$X = A'.B' + A'.B.C'$$

$$X = A'.(B' + B.C')$$

$$X = A'.(B'.(C+C') + B.C')$$

$$X = A'.(B'C + B'C' + B.C')$$

$$X = A'.(B'C + B'C' + B'C' + B.C')$$

$$X = A'.(B'(C+C') + C'(B'+B))$$

$$X = A'(B' + C')$$

$$X = A'B' + A'C'$$

See why we use K-maps?


L05: Reduction Techniques

9

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

K-maps

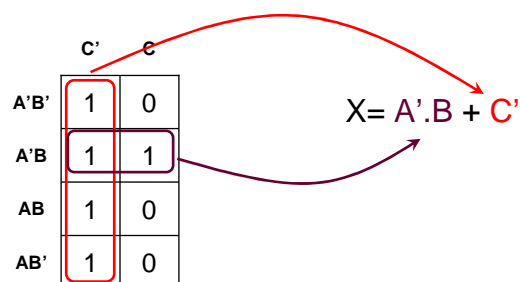- Try to encircle as many 1s as possible:



L05: Reduction Techniques

10

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

K-maps

- Pick the greatest number of ones on each oval.
Remember the number of ones has to be 1,2,4,8,etc.

	C'D'	C'D	CD	CD'
A'B'	0	0	0	0
A'B	1	1	1	0
AB	1	1	1	0
AB'	0	0	0	0

Six ones encircled is not valid.

L05: Reduction Techniques

11

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

K-maps

- Pick the greatest number of ones on each oval.
Remember the number of ones has to be 1,2,4,etc.

	C'D'	C'D	CD	CD'
A'B'	0	0	0	0
A'B	1	1	1	0
AB	1	1	1	0
AB'	0	0	0	0

Not optimal.

L05: Reduction Techniques

12

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

K-maps

- Pick the greatest number of ones on each oval.
Remember the number of ones has to be 1,2,4,etc.

	C'D'	C'D	CD	CD'
A'B'	0	0	0	0
A'B	1	1	1	0
AB	1	1	1	0
AB'	0	0	0	0

Not optimal.

L05: Reduction Techniques

13

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

K-maps

- Pick the greatest number of ones on each oval.
Remember the number of ones has to be 1,2,4,etc.

	C'D'	C'D	CD	CD'
A'B'	0	0	0	0
A'B	1	1	1	0
AB	1	1	1	0
AB'	0	0	0	0

Optimal!

$$X = B.C' + B.D$$

L05: Reduction Techniques

14

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

K-maps

- Remember: two cells are adjacent if only one variable changes... So for this K-map:

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B	0	0	0	0
AB	1	0	0	1
AB'	1	1	1	1

$X = B' + A.D'$

L05: Reduction Techniques

15

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

K-maps

- I mentioned before that you can rearrange the rows/columns so far only one variable changes at a time. Then the problem from the previous slide can be redrawn as:

	C'D	CD	CD'	C'D'
A'B	0	0	0	0
AB	0	0	1	1
AB'	1	1	1	1
A'B'	1	1	1	1

$X = B' + A.D'$

WARNING: super easy to do in the computer (cut & paste rows/columns). A pain to do in paper by hand!

L05: Reduction Techniques

16

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 1

- Simplify the following equation using a K-map:
 $X = A'.D' + A.B'.D' + A'C'D + A'.C.D$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B	1	1	1	1
AB	0	0	0	0
AB'	1	0	0	1

Cells with A'.D'

Cells with A.B'.D'

Cells with A'.C'.D

Cells with A'.C.D

L05: Reduction Techniques

17

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 1

- Simplify the following equation using a K-map:
 $X = A'.D' + A.B'.D' + A'C'D + A'.C.D$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B	1	1	1	1
AB	0	0	0	0
AB'	1	0	0	1

→ A'

Four corners: B'.D'

$$X = A' + B'.D'$$

L05: Reduction Techniques

18

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 1

- For your amusement, the previous K-map has been rolled one row and one column, just in case you can visualize the adjacency of the four corners...

	C'D	CD	CD'	C'D'
AB'	0	0	1	1
A'B'	1	1	1	1
A'B	1	1	1	1
AB	0	0	0	0

$$X = A' + B'D'$$

Don't do this. It is a waste of time!

L05: Reduction Techniques

19

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

POS simplification with K-maps

- Instead of working with the ones work with the zeroes.
- You'll get F' .
- Use De Morgan's theorem to find F .
- Example next slide...

L05: Reduction Techniques

20

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

POS simplification with K-maps

	C'D'	C'D	CD	CD'
A'B'	1	1	0	1
A'B	0	1	0	0
AB	0	0	0	0
AB'	1	1	0	1

$$F' = B.D' + AB + CD$$

De Morgan's says

$$(X.Y)' = X' + Y'$$

Or

$$X.Y = (X' + Y')'$$

$$F' = (B' + D)' + (A' + B')' + (C' + D')'$$

$$F' = ((B' + D).(A' + B').(C' + D'))'$$

$$F = (B' + D).(A' + B').(C' + D')$$

L05: Reduction Techniques

21

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 2

- Get the product of sums from the K-map below:

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B	1	0	0	1
AB	1	0	0	1
AB'	0	1	1	1

$$F' = B.D + AB'C'D'$$

$$F = (B' + D').(A' + B + C + D)$$

L05: Reduction Techniques

22

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Don't Care Conditions

- If the Boolean function has un-specified outputs, you can make them either 0 or 1 at your convenience!
- One classical example is the conversion of a BCD to 7-segment displays. The inputs $(1010)_2$ to $(1111)_2$ have un-specified outputs.


L05: Reduction Techniques

23

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: BCD to 7-Segments

Inputs				Outputs						
D	C	B	A	F _a	F _b	F _c	F _d	F _e	F _f	F _g
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	0	0	1	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	0	1	0	0
0	1	1	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	1	0	0
1	0	1	0	?	?	?	?	?	?	?
1	0	1	1	?	?	?	?	?	?	?
1	1	0	0	?	?	?	?	?	?	?
1	1	0	1	?	?	?	?	?	?	?
1	1	1	0	?	?	?	?	?	?	?
1	1	1	1	?	?	?	?	?	?	?

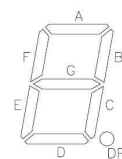

Don't Care!

Some people / books use 'x' or 'd' for don't cares

24

L05: Reduction Techniques

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Solution for Segment 'a'

D	C	B	A	F _a
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	C'D'	C'D	CD	CD'
A'B'	0	0	?	1
A'B	0	?	?	0
AB	0	?	?	0
AB'	1	0	?	0

$$F_a = A \cdot B' \cdot C' \cdot D' + A' \cdot B' \cdot C$$

L05: Reduction Techniques

25

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Solution for Segment 'b'

D	C	B	A	F _b
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	C'D'	C'D	CD	CD'
A'B'	0	0	?	0
A'B	0	?	?	1
AB	0	?	?	0
AB'	0	0	?	1

$$F_b = A'BC + AB'C$$

L05: Reduction Techniques

26

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Solution for Segment 'c'

D	C	B	A	F _c
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	C'D'	C'D	CD	CD'
A'B'	0	0	?	0
A'B	1	?	?	0
AB	0	?	?	0
AB'	0	0	?	0

$$F_c = A'.B.C'$$

L05: Reduction Techniques

27

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Solution for Segment 'd'

D	C	B	A	F _d
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	C'D'	C'D	CD	CD'
A'B'	0	0	?	1
A'B	1	?	?	0
AB	0	?	?	1
AB'	0	0	?	0

$$F_d = A'.B.C' + A'.B'.C + A.B.C$$

L05: Reduction Techniques

28

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Solution for Segment 'e'

D	C	B	A	F_e
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	$C'D'$	$C'D$	CD	CD'
$A'B'$	0	0	?	1
$A'B$	0	?	?	0
AB	1	?	?	1
AB'	1	1	?	1

Finally!

$$F_e = A + B' \cdot C$$

L05: Reduction Techniques

29

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Solution for Segment 'f'

D	C	B	A	F_f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	$C'D'$	$C'D$	CD	CD'
$A'B'$	0	0	?	0
$A'B$	1	?	?	0
AB	1	?	?	1
AB'	1	0	?	0

$$F_f = B \cdot C' + A \cdot B + A \cdot C' \cdot D'$$

L05: Reduction Techniques

30

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 3: Solution for Segment 'g'

D	C	B	A	F _g
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	C'D'	C'D	CD	CD'
A'B'	1	0	?	0
A'B	0	?	?	0
AB	0	?	?	1
AB'	1	0	?	0

$$F_g = B'.C'.D' + A.B.C$$

You are welcome!

L05: Reduction Techniques

31

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Universal Gates

- An universal gate is a gate that can be used to implement any logic function. There are two universal gates:
 - NAND
 - NOR


L05: Reduction Techniques

32

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Universal Gate: NAND

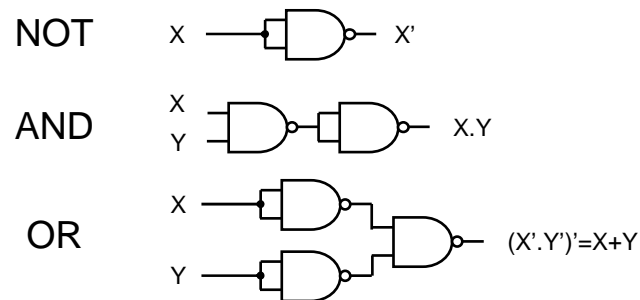- We need to show that we can implement a NOT, AND, and OR with just NAND gates:




L05: Reduction Techniques

33

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

The AND-OR Circuit

These three circuits
behave the same!

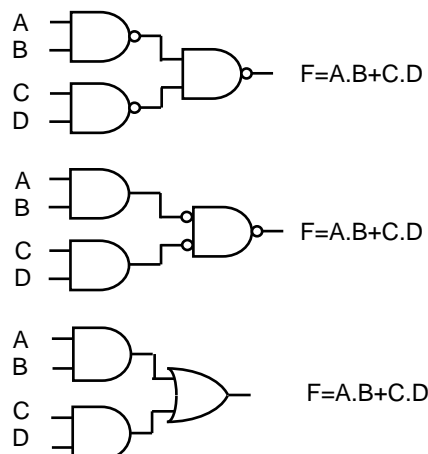


L05: Reduction Techniques

34

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Universal Gate: NOR

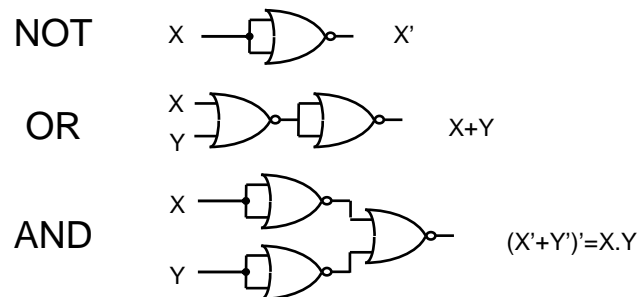- We need to show that we can implement a NOT, AND, and OR with just NOR gates:



L05: Reduction Techniques

35

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 4: All NAND Design

- Consider the Boolean equations for the 2-bit to 7-segment decoder from last lecture. Implement the circuit using only NAND gates. Simulate in Multisim.


- $F_a = F_d = X'.Y$
- $F_b = 0$
- $F_c = X.Y'$
- $F_e = Y$
- $F_f = X+Y$
- $F_g = X'$

L05: Reduction Techniques

36

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Example 4: All NAND Design

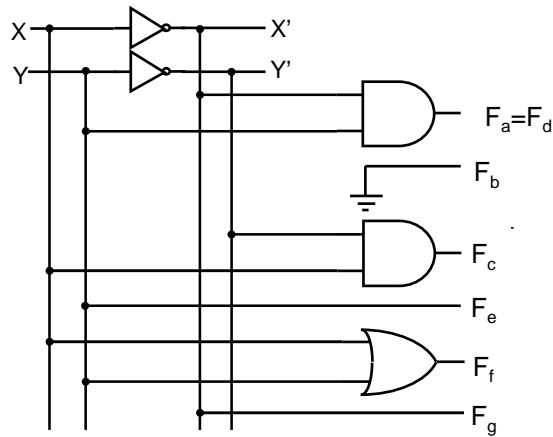


The original circuit

L05: Reduction Techniques

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

37

Example 4: All NAND Design

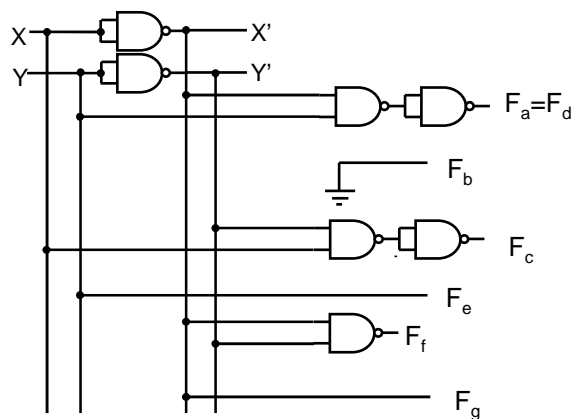


The all-NAND circuit

L05: Reduction Techniques

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

38

Multisim Simulation

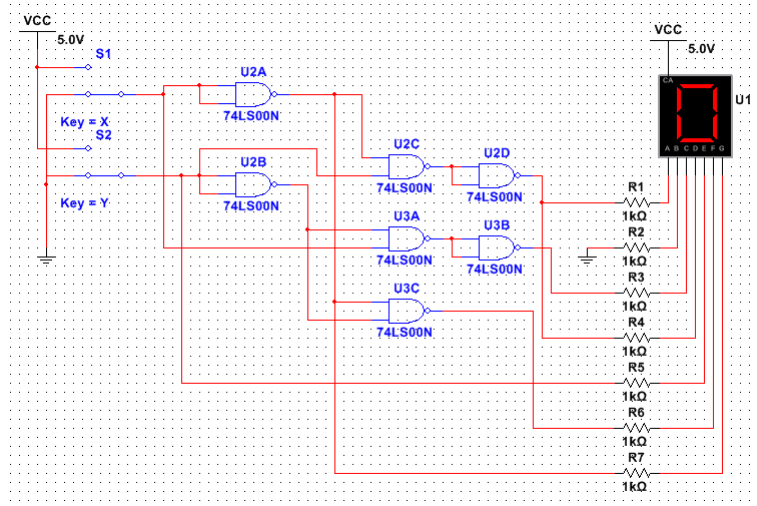

L05: Reduction Techniques

39

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Exercises

- Simplify the Boolean equation

$$Y = L.T.P + L'.T.W + L'.T'.P + L'.W'.T$$
 Using a K-map. Implement the simplified circuit of the equation above using NOR gates only.
- Design a circuit, using a K-map, that detects a number divisible by 3 in the range 1 to 15 (zero is don't care). Implement the circuit using NAND gates only.

L05: Reduction Techniques

40

Copyright © 2009-2019, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.