

# THE UNIVERSITY OF BRITISH COLUMBIA

## Department of Electrical and Computer Engineering

### EECE 373: Electromechanical Energy Conversion and Transmission

#### Final Exam December 11, 2004

Magnetic Circuits, Transformers, DC Machines, Induction Machines, and Synchronous Machines

Surname: \_\_\_\_\_

First Name: \_\_\_\_\_

Student ID: \_\_\_\_\_


Signature: \_\_\_\_\_

- **Close notes and books.**
- You are allowed to have only a **calculator** and a **pen/pencil**.
- Show your work including **derivations, comments, assumptions**, and **units** wherever appropriate.
- Use back side of each page or ask for additional pages if you need extra space to write your answers.
- Exams suspected of cheating and/or turned in late will not be marked – **failed exam**.
- Cheating may result in your suspension and/or withdrawal from the university
- You have **90** minutes to answer the following questions:



Problem	Points	Max.
1		20
2		20
3		20
4		20
5		20
Total		100
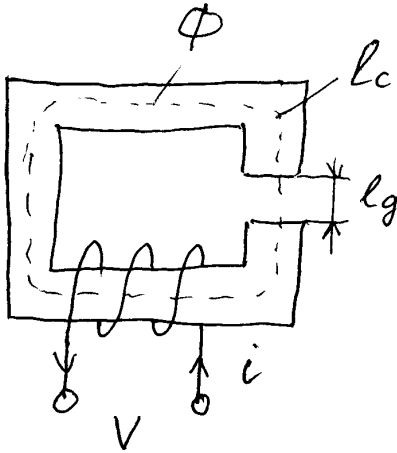
### Problem 1 (20pts)

Consider the magnetic system shown below. The core and air-gap have reluctances are  $\mathcal{R}_c = 0.5 \times 10^6 \text{ At/Wb}$  and  $\mathcal{R}_g = 4.5 \times 10^6 \text{ At/Wb}$ , respectively. The cross-sectional area of the core and air-gap is  $A_c = A_g = 2.3 \text{ cm}^2$ . Neglect flux leakage, fringing, and core losses. The dc resistance of the coil is  $3 \Omega$ . The coil is connected to a 60Hz ac source which provides  $V = 25 \text{ V}$  (rms) and the resulted current is  $I = 5 \text{ A}$  (rms).



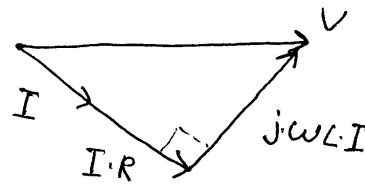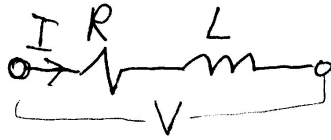- (5pts) Draw an equivalent **electric** circuit and sketch the corresponding qualitative phasor diagram
- (5pts) Calculate the inductance  $L$  and the number of turns  $N$  (round it to the closest integer)
- (5pts) Calculate the flux  $\Phi$  (rms value)
- (5pts) Calculate the flux density in the air-gap  $B_g$  (rms value)



b)  $V = 25 \text{ V}$ ;  $I = 5 \text{ A}$ ;  $R = 3 \Omega$

$$Z = V/I = 25/5 = 5 \Omega$$

$$X = \sqrt{Z^2 - R^2} = \sqrt{25 - 9} = 4 \Omega$$

$$L = X/\omega = \frac{4}{60 \cdot 2\pi} = \boxed{0.0106 \text{ H}}$$

$$N \cdot I = F = \Phi \cdot (\mathcal{R}_g + \mathcal{R}_c)$$

$$L = \frac{N^2}{\mathcal{R}_g + \mathcal{R}_c}$$

$$N = \sqrt{L \cdot (\mathcal{R}_g + \mathcal{R}_c)} \approx \boxed{230}$$

c)  $\Phi = \frac{F}{\mathcal{R}_g + \mathcal{R}_c} = \frac{N \cdot I}{\mathcal{R}_g + \mathcal{R}_c} = \frac{230 \cdot 5}{5 \times 10^6} = \boxed{2.3 \times 10^{-4} \text{ Wb}}$

d)  $\Phi = B \cdot A \Rightarrow B = \frac{\Phi}{A_c} = \frac{2.3 \times 10^{-4}}{2.3 \times 10^{-4}} = \boxed{1 \text{ T}}$

## Problem 2 (20pts)


Consider a single-phase 120V, 60Hz transformer with the following parameters:  $R_1 = 1 \Omega$ ,  $X_1 = 2 \Omega$ ,  $X_m = 100 \Omega$ ,  $R_c = 200 \Omega$ ,  $R_2 = 1 \Omega$ , and  $X_2 = 2 \Omega$ , respectively. Assume that both windings have the same number of turns. Assume **T-equivalent circuit** in the following questions:

- (a) (5pts) Sketch the equivalent circuits and label its parameters and variables (just the symbols)  
 (b) (8pts) Assume an Open-Circuit Test wherein the primary winding is supplied from a 120V ac source.

Calculate primary current  $I_{1,oc}$ , power real  $P_{oc}$ , and secondary voltage  $V_{2,oc}$

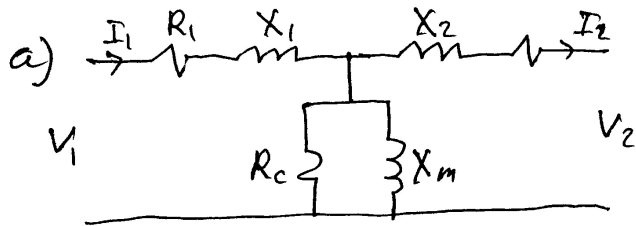- (c) (7pts) Assume a Short-Circuit Test. As you know, the Short-Circuit Test should be performed at reduced voltage in order to avoid very high currents. Assume that a maximum allowable primary current is

$I_{1,max} = I_{1,sc} = 5A$ , calculate the required primary voltage  $V_{1,sc}$ , and real power  $P_{sc}$



$$Z_1 = R_1 + jX_1 = 1 + j2$$

$$Z_2 = R_2 + jX_2 = 1 + j2$$

$$Z_m = \frac{jX_m \cdot R_c}{jX_m + R_c} = 40 + j80$$

b) OCT

$$I_{1,oc} = \frac{V_1}{Z_1 + Z_m} = \frac{120}{41 + j82} = 0.5854 - j1.17 = 1.31 A_{rms}$$

$$I_{1,oc} = 1.31 \angle -63.435^\circ; \quad PF = \cos(63.435^\circ) = 0.4472$$

$$V_{2,oc} = I_{1,oc} \cdot Z_m = 117.07 V_{rms}$$

$$P_{oc} = V_1 \cdot I_{1,oc} \cdot \cos \varphi = V_1 \cdot \text{real}(I_{1,oc}) = 120 \cdot 0.5854 = 70.2 W$$

c) SCT

$$Z_{sc} = Z_1 + \frac{Z_2 \cdot Z_m}{Z_2 + Z_m} = 1.976 + j3.951$$

$$|Z_{sc}| = 4.4176 \Omega; \quad I_{1,sc} = 5 A_{rms}$$

$$V_{1,sc} = |Z_{sc}| \cdot I_{1,sc} = 22.09 V_{rms}$$

$$I_{1,sc} = \frac{V_{1,sc}}{Z_{sc}} = 2.2361 - j4.472 = 5 A_{rms}$$

$$P_{sc} = V_{1,sc} \cdot I_{1,sc} \cdot \cos \varphi = V_{1,sc} \cdot \text{real}(I_{1,sc}) = 22.09 \cdot 2.2361 = 49.4 W$$

$$I_{2,sc} = \frac{V_{1,sc} - I_{1,sc} \cdot Z_1}{Z_2} = 2.1815 - j4.363 = 4.87 A_{rms}$$

**Problem 3 (20pts)**


Consider a 120V **Shunt DC Motor** with the following parameters  $R_a = 0.5 \Omega$ ,  $R_f = 200 \Omega$ . When the machine is connected to a 120V dc source it draws the armature current  $I_a = 10A$  and the shaft speed is  $n = 1800 \text{ rpm}$  CCW under a given mechanical load. The friction losses are  $P_{fric} = 50W$

(a) (5pts) Sketch the equivalent steady-state electric circuit and label all parameters and variables

(b) (5pts) Determine the generated voltage  $E_a$

(c) (5pts) Determine the load torque  $T_m$  and its direction (circle CW or CCW)

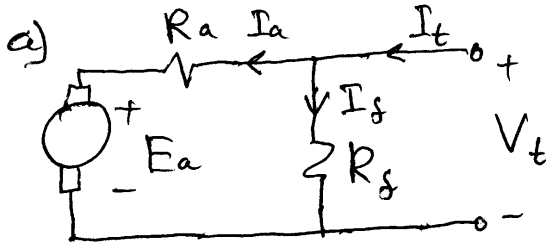(d) (5pts) Determine the efficiency of the motor  $\eta$



b)

$$E_a = V_t - R_a \cdot I_a =$$

$$= 120 - 0.5 \cdot 10 = \boxed{115V}$$

c)

$$\omega = n \cdot \frac{\pi}{30} = 188.496 \text{ rad/s}$$

$$P_e = E_a \cdot I_a = 1150 \text{ W}$$

$$P_m = P_e - P_{fric} = 1150 - 50 = 1100 \text{ W}$$

$$P_m = T_m \cdot \omega \Rightarrow T_m = \frac{P_m}{\omega} = \frac{1100}{188.496} = \boxed{5.84 \text{ N.m}}$$

CW

d)

$$\eta = \frac{P_{out}}{P_{in}}$$


$$P_{out} = P_m ; P_{in} = V_t \cdot I_t = V_t \cdot \left( I_a + \frac{V_t}{R_f} \right) = 120 \cdot (10 + 0.6)$$

$$= 1272 \text{ W}$$

$$\eta = \frac{1100}{1272} = 0.865 = \underline{\underline{86.5\%}}$$


#### Problem 4 (20pts)

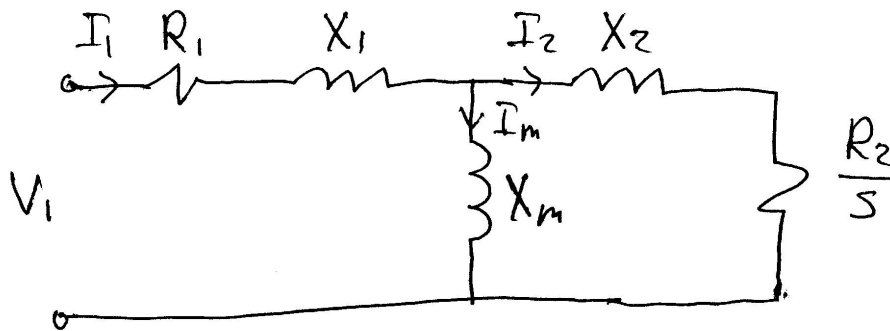- (a) (10pts) Sketch a per-phase equivalent circuit of an Induction Machine (IEEE Recommended, most commonly used) and label all elements and variables.



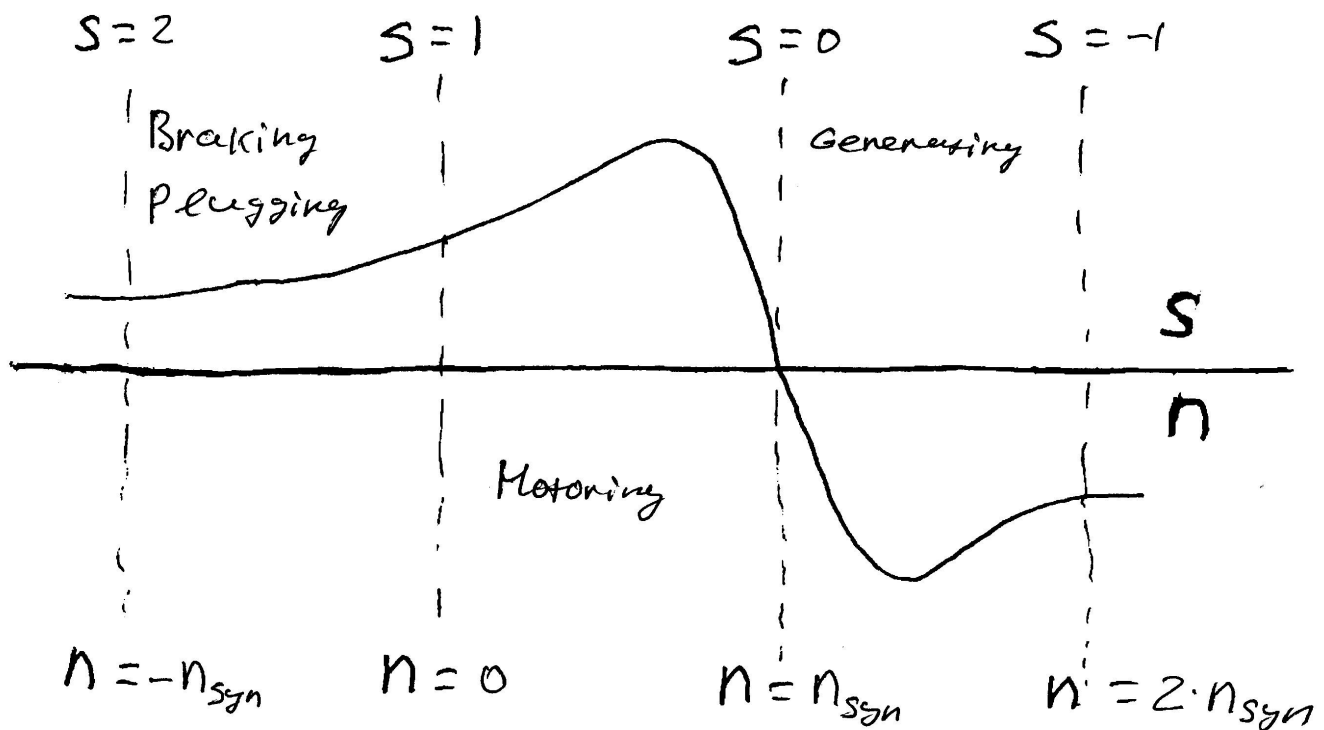- (b) (10pts) Consider a typical Torque-Speed Characteristic of an Induction machine shown below.


- (4pts) Identify and label the regions corresponding to the three modes of operation
- (3pts) Label the slip values (assume integers)
- (3pts) Label the speed values ( $\pm n_{syn}, 0$ , etc.)



**Problem 5 (20pts)**

Consider a 3-phase, 60Hz, 208V (line-to-line) 2-pole **Permanent Magnet Round-Rotor Synchronous Generator** with the following parameters: Rated (nominal) output electrical power  $S_{3\phi} = 1.2\text{kVA}$ , per-phase stator resistance and synchronous reactance are  $R_a = 1\Omega$  and  $X_s = 20\Omega$ , respectively. Assume that a nominal load with 0.7 lagging power factor is connected to the generator terminals.

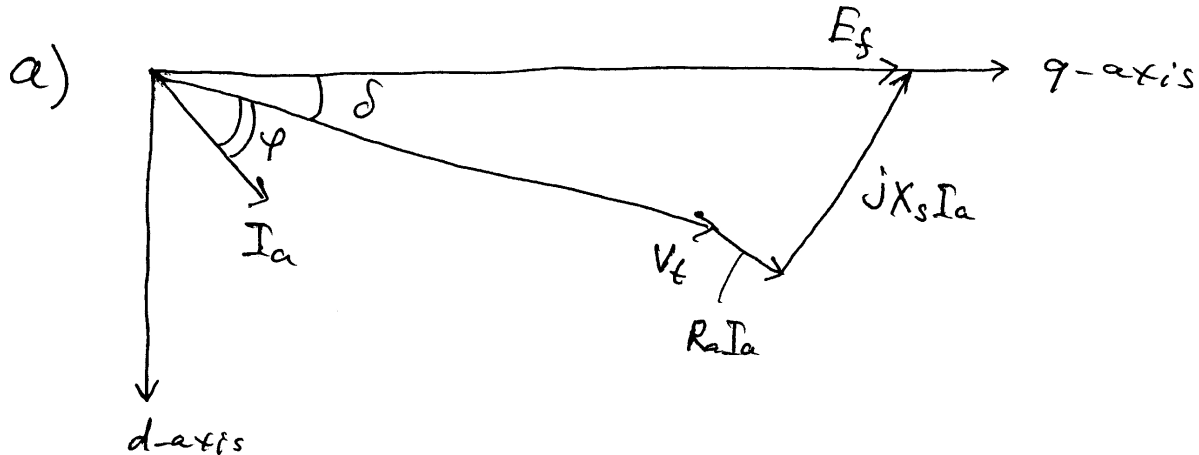- (a) (6pts) Sketch a phasor diagram and label the q- and d- axes, all relevant angles, and phasors  
 (b) (7pts) Calculate the induced voltage  $E_f$  and the rotor angle  $\delta$  in degrees  
 (c) (7pts) Assume mechanical rotational losses  $P_{\text{mech\_loss}} = 50\text{W}$ , calculate the efficiency  $\eta$



$$b) \quad E_f = V_t + (R_a + jX_s)I_a$$

$$I_a = \frac{S}{\sqrt{3} \cdot V_{\text{line}}} = \frac{1200}{\sqrt{3} \cdot 208} = 3.331 \text{ A (rms)}$$

$$\varphi = \arccos(\text{PF}) = \arccos(0.7) = 45.57^\circ$$

$$I_a = 3.331 \angle -45.57^\circ = 2.3316 - j \cdot 2.3787 \text{ A}$$

$$E_f = \frac{208}{\sqrt{3}} + (1 + j20) \cdot (2.3316 - j \cdot 2.3787)$$

$$= 160.99 + j44.253 = 175.66 \angle +14.59$$

$$\delta = 14.59 \text{ degrees}$$

$$c) \quad P_{\text{out}} = S \cdot \text{PF} = 1200 \cdot 0.7 = 840 \text{ W}$$

$$P_{\text{in}} = P_{\text{out}} + P_{\text{mech\_loss}} + 3 \cdot R_a \cdot I_a^2 = 923.3 \text{ W}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = 0.91 = 91\%$$