

**THE UNIVERSITY OF BRITISH COLUMBIA**  
**Department of Electrical and Computer Engineering**  
**EECE 365: Applied Electronics and Electromechanics**

**Final Exam / Sample-Practice Exam**  
**Spring 2008**  
**April 23**

Topics Covered: Magnetic Circuits, Electromechanical Devices with Motion, DC Motors, AC Power and Transformers, Induction Motors, Synchronous Motors, Brushless DC Motors, Stepper Motors

Surname: \_\_\_\_\_

First Name: \_\_\_\_\_

Student ID: \_\_\_\_\_


Signature: \_\_\_\_\_

- **Close notes and books.**
- You are allowed to have only a **calculator**, a **pen/pencil**, and **two double-sided pages of hand-written formulas**.
- Show your work including **derivations**, **comments**, **assumptions**, and **units** wherever appropriate.
- Use back side of each page or ask for additional pages if you need extra space to write your answers.
- Exams suspected of cheating and/or turned in late will not be marked – **failed exam**.
- You have **90** minutes to answer the following questions:

Problem	Points	Max.
1		
2		
3		
4		
5		
6		
7		
8		
9		
Total		100

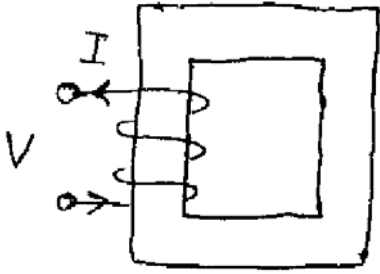**Problem 1:**


Consider the magnetic system shown below. The core has permeability and dimensions such that the reluctance of magnetizing path is  $\mathfrak{R}_m = 10^5 \text{ At/Wb}$ . The coil has 100 turns, dc resistance of  $3 \Omega$ , and is connected to a dc source  $V_{dc} = 12 \text{ V}$ . It is also known that 10% of the total flux  $\Phi$  produced by the coil leaks into the air.



- (a) Draw an equivalent **magnetic** circuit, show the direction of mmf and the fluxes
- (b) Calculate flux linkage  $\lambda$ , and inductance  $L$
- (c) Find the rms value of current if the coil is supplied from an ac source  $V_{ac} = 12 \text{ V}(rms)$  with the frequency  $f_e = 5.093 \text{ Hz}$

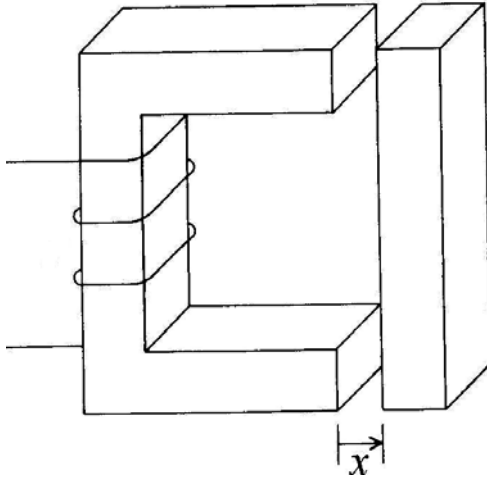**Problem 2:**

Consider an electro-mechanical device shown in the figure. You can use common approximations as we did in class and assume magnetically-linear core. The air-gap between the core and the plunger is denoted by  $x$  (which has units of meters). Assume that total inductance of this device may be approximated as  $L(x) = 0.15 + \frac{5 \cdot 10^{-6}}{x^2}$  H, and the dc resistance  $r$  is  $20\ \Omega$ .



- (a) Sketch the equivalent **magnetic** circuit and label all elements
- (b) Sketch the equivalent **electric** circuit and label all elements
- (c) Express the electromagnetic force  $f_e(x, I_{dc})$
- (d) What value of dc voltage  $V_{dc}$  and dc current  $I_{dc}$  should be applied to the coil in order to produce a force of  $25\text{ Nm}$  when the plunger has air-gap of  $2\text{ mm}$ ?
- (e) Calculate the energy stored in the system for part (d)

**Problem 3:**

Consider a **Permanent-Magnet DC motor** with the following parameters: rated voltage  $V_t = 240 \text{ V}$ ; armature resistance  $R_a = 1.2 \Omega$ , and friction torque  $T_{fric} = 0.5 \text{ Nm} = \text{const}$ .

- (a) When the motor drives a mechanical load of  $9.5 \text{ Nm}$  it draws a current of  $10 \text{ A}$ . Calculate the induced armature emf  $E_a$  and torque constant  $K_t$
- (b) Assume that mechanical load has increased to  $T_m = 19.5 \text{ Nm}$ . Calculate the motor speed  $n$  in rpm, speed regulation  $SR$  in %, and efficiency  $\eta$  also in %

**Problem 4:**

Consider a 115V series-connected DC motor with the following parameters: armature resistance  $R_a = 1\Omega$ ; and field winding resistance  $R_f = 2\Omega$ . The motor is supplied from a dc source  $V_t = 115\text{ V}$  and is operating under nominal load at speed  $n = 3000\text{ rpm}$  drawing armature current  $I_a = 5\text{ A}$ .

- (a) Draw an equivalent circuit
- (b) Calculate the induced back emf,  $E_a$
- (c) Calculate the torque at zero speed (starting torque),  $T_{start}$

**Problem 5:**

A 1.5-kVA, 60-Hz, step-up transformer has two windings with  $N_1 = 1000$  and  $N_2 = 2000$  turns, respectively. The leakage reactances are  $X_1 = 2\Omega$ ,  $X_2 = 8\Omega$  (each quantity is referred to its own side), and the magnetizing reactance  $X_{m2} = 400\Omega$  (referred to the secondary side). The core and copper losses can be ignored. Assume 120V is applied to the primary side:

- (a) Calculate the open-circuit primary current  $I_{1,oc}$  and the secondary voltage  $V_{2,oc}$  (their rms values)
- (b) Assume a resistive load  $R_{Load} = 40\Omega$  is connected to the secondary side. Calculate the resulting currents (rms) in each winding. Also calculate the input power-factor angle  $\phi$  in degrees

**Problem 6:**

Consider a 60Hz, 208V (line-to-line), Y-connected, NEMA Class B Squirrel-Cage Induction Motor with the following per-phase parameters:  $R_1 = 1\ \Omega$ ,  $R_2 = 1.5\ \Omega$ ,  $X_1 = X_2 = 3\ \Omega$ , and  $X_m = 40\ \Omega$  (all referred to the stator). The motor is supplied with the nominal (rated) voltage and is driving a mechanical load. The speed of the motor shaft is  $n = 855$  rpm. You can neglect core losses and use an approximate equivalent circuit. Recall that

$$T_e = 3 \frac{1}{\omega_{syn}} \cdot (I_2)^2 \cdot \frac{R_s}{s}. \text{ Determine the following:}$$

- (a) Number of poles  $P$  and slip  $s$
- (b) Input stator current  $I_1$ , power factor PF, and total three-phase input power  $P_{in}$
- (c) Developed electromagnetic torque  $T_e$
- (d) Assume the friction torque is 5% of the developed torque  $T_e$ . Calculate the useful mechanical load torque  $T_m$  and the motor efficiency  $\eta$  in %

**Problem 7:**

Consider a 3-phase, 60Hz, 208V (line-to-line) 14-pole **Permanent Magnet Round-Rotor Synchronous Motor** with the following parameters: per-phase stator resistance and synchronous reactance are  $R_a = 1\Omega$  and  $X_s = 10\Omega$ , respectively. Assume that the motor outputs mechanical power  $P_m = 1676\text{W}$  and power factor is one.



- (a) Sketch an equivalent **electric circuit** (per-phase)
- (b) Calculate the motor shaft is  $n$  in rpm, induced voltage  $E_f$ , and the rotor angle  $\delta$  in degrees
- (c) Assume mechanical rotational losses  $P_{mech\_loss} = 50\text{W}$ , calculate the efficiency  $\eta$



**Problem 8:**

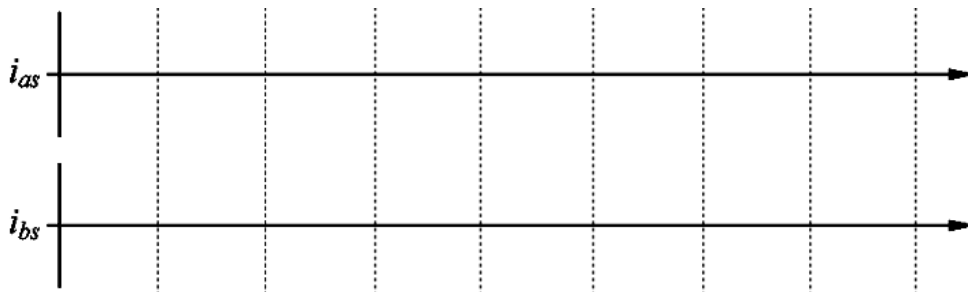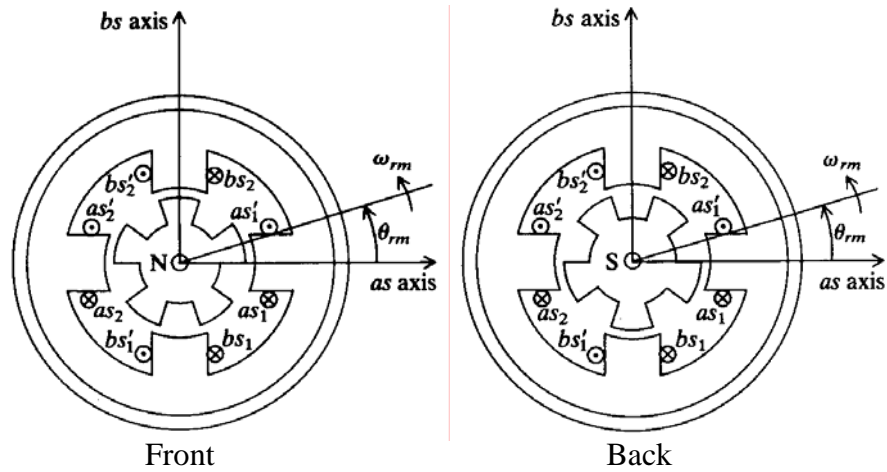(a) Consider a 2-phase **PM Stepper Motor** shown here. The rotor initial position is as shown corresponds to the phase ***bs*** energized.

Sketch the sequence of currents  $i_{as}$  and  $i_{bs}$  to drive this motor at **half-step** in **CW** direction assuming phase ***bs*** is energized first to positive value.




(b) Assume a standard (one phase energized at a time) full-step operation with duration of current pulses  $T_{step} = 1/f_{step} = 0.01\text{sec}$ . Calculate rotor mechanical speed  $n$  in rpm

(c) List all classes/types of stepper motors that we discussed in class:

(d) List some of the factors that limit the stepping rate (or speed) at which a given stepper motor can operate: We discussed this in class and you have observed that in Lab-5.

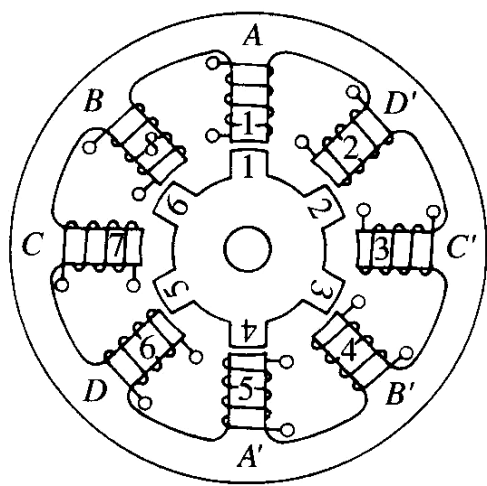**Problem 9:**

Consider a single-stack stepper motor shown below. Complete the following table:



2pts	Stator tooth pitch	
2pts	Rotor tooth pitch	
3pts	Step length	
3pts	Number of steps per revolution (Resolution)	
3pts	Assume sequence of pulses as B – C – D – A, determine the direction of rotation ( <b>CW</b> or <b>CCW</b> )	
3pts	Assume you have a 4-phase pulse generator to supply this motor. The generator produces 12 pulses per second per phase (48 pulses per second total). What is the motor speed in <b>rpm</b> ?	